

Problem-Set #1 – COE838

Introduction and SystemC


Q-1. Suppose we have four different processors; each does 25% of the application. If we improve two of the processors by 10 times, what would be the overall application speedup?

Q-2. Write a SystemC module to model a D-type flip-flop.

Q-3. Identify the main function of the following SystemC module. Explain the module briefly.

```
SC_MODULE(what) {
    sc_in<bool> clk;
    sc_out<bool> dout1;
    sc_out<bool> dout2;
    sc_signal<bool> sig1;
    bool var2;
    void p1() { // using signals
        sig1.write(!sig1.read());
        dout1.write(sig1.read());
    }
    void p2() { // using variables
        var2 = !var2;
        dout2.write(var2);
    }
}
SC_CTOR(what) {
    sig1.write(true); // init
    var2=false; // init
    SC_METHOD(p1);
    sensitive << clk.pos();
    dont_initialize();
    SC_METHOD(p2);
    sensitive << clk.pos();
    dont_initialize();
}
};
```

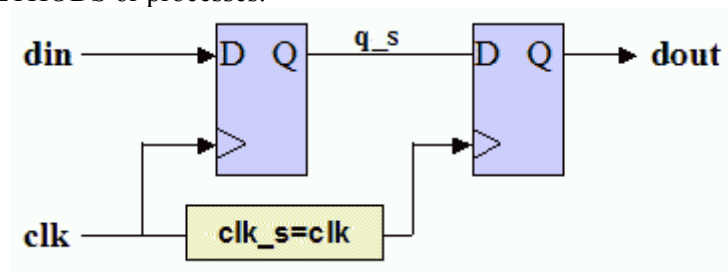Q-4. Model the following two flip-flop hardware, by writing the SystemC code as a module. The module can have multiple METHODS or processes.



Q-5. SystemC code of a counter module is given below. Identify the type of counter and which signal it counts. Justify your answer.

```
#include "systemc.h"
SC_MODULE (which_counter) {
    //-----Input Ports-----
    sc_in  <bool> enable, clk, reset;
    //-----Output Ports-----
    sc_out <sc_uint<8>> out;
    //-----Internal Variables-----
    sc_uint<8> count;

    //-----Code Starts Here-----
    void counter () {
        if (reset.read()) {
            count = 0 ;
        } else if (enable.read()) {
            count = count + 1;
        }
        out.write(count);
    }

    SC_CTOR(which_counter) {
        SC_METHOD (counter);
        sensitive << clk.pos();
    }
};
```

Q-6. Design and write the SystemC code of a down-counter module that will initialize its count at 1024 and then count the number of input pulses.

Q-7. Design and write the SystemC code for asynchronous read/write random access memory (RAM) module. The memory size is 512 bytes, and the word size of the memory is of 16-bits. The memory has separate data-in and data-out ports of 16-bits each. In addition to memory address signals, the memory module has chip select (cs), output enable (oe) and write enable (we) input signals.