

MIPS-Lite CPU Microprogram- based Control

COE608: Computer Organization and Architecture

Dr. Gul N. Khan

<http://www.ee.ryerson.ca/~gnkhan>

Electrical and Computer Engineering

Ryerson University

Overview

- Introduction
- MIPS Multicycle Datapath
- Multicycle Control
- Microprogrammed Control Unit
- Control Unit Design Steps
- Microprogramming for the Control Unit

Partially from Chapter 4 of the text book


Multicycle Approach

- We will be reusing the functional units.
 - ◆ ALU used to compute address & increment PC.
 - ◆ Memory used for instruction and data.
- Control signals will not be determined solely by the instructions
- Control unit design by using classical FSM design is impractical due to large number of inputs and states it may have.
- An extension to the classical approach is used by experienced designer in designing control logic circuits:
 - ◆ Sequence register and decoder method.
 - ◆ One flip-flop per state method.
 - ◆ Microprogram controller.
 - ◆ PLA controller.

The PLA and micro-program control uses PLD and ROM/PROM.

Modification of PROM or replacing the ROM modifies the micro-program control.


Single Cycle Datapath

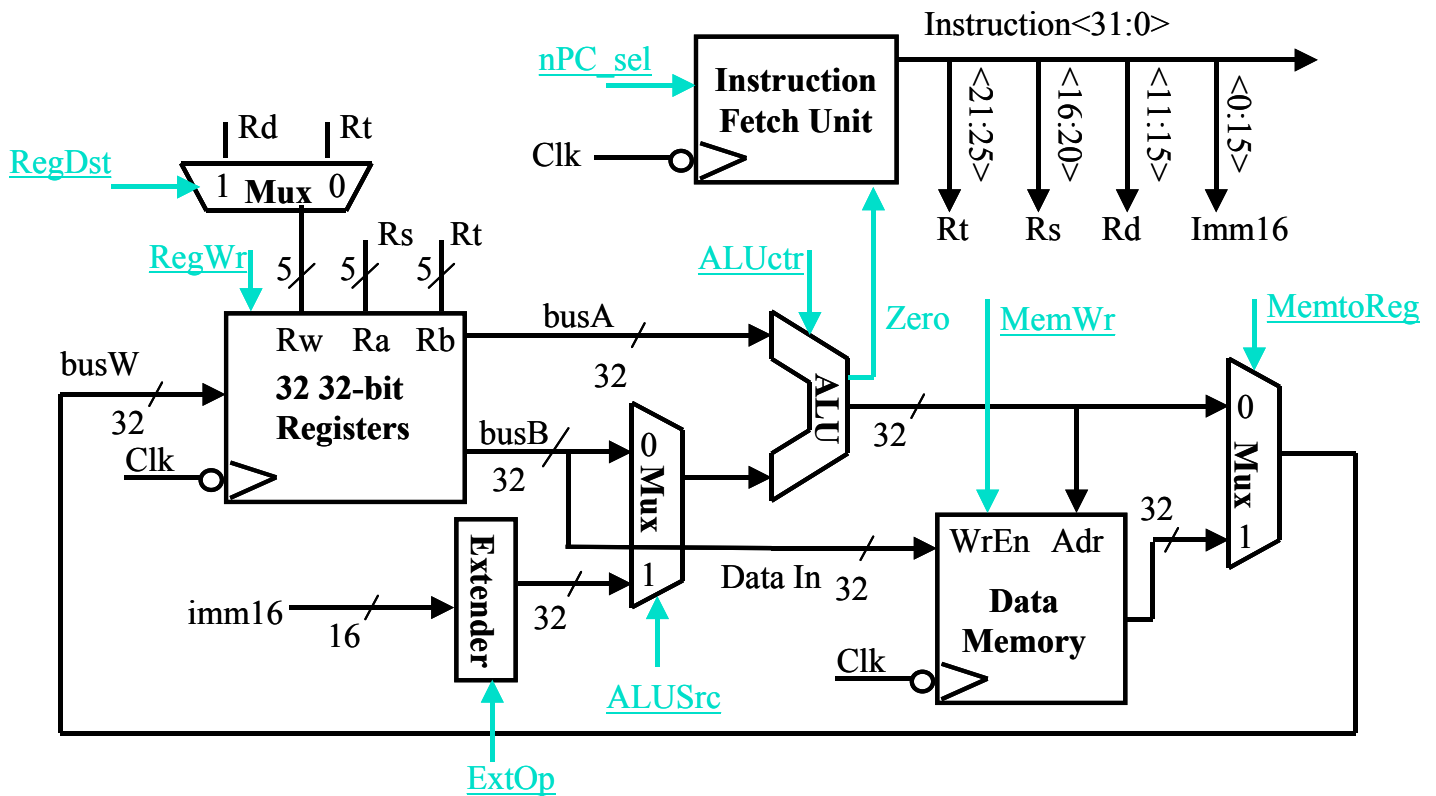

Long Cycle Time

- All instructions take as much time as the slowest.
- Real memory is not like our idealized memory
Cannot always get the job done in one (short) cycle


Arithmetic & Logical

 

Load



Store

 


Branch




Single Cycle Control

op	00 0000		10 0011	10 1011	00 0100	00 0010
	R-type		lw	sw	beq	jump
RegDst	1		0	x	x	x
ALUSrc	0		1	1	0	x
MemtoReg	0		1	x	x	x
RegWrite	1		1	0	0	0
MemWrite	0		0	1	0	0
Branch	0		0	0	1	0
Jump	0		0	0	0	1
ALUop (Symbolic)	“R-type”		Add	Add	Subtract	xxx
ALUop <1>	1		0	0	0	x
ALUop <0>	0		0	0	1	x

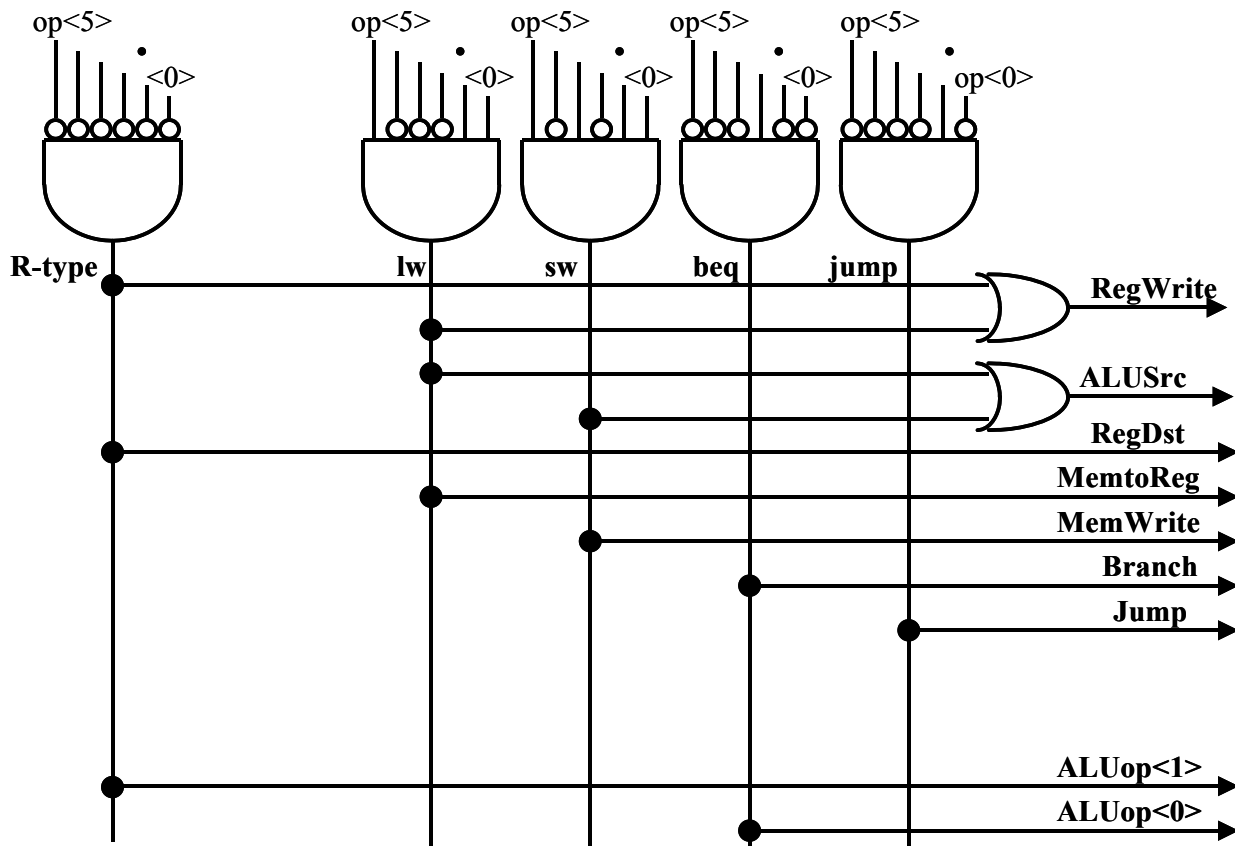

Multiple Cycle Datapath

Minimizes Hardware:
One memory

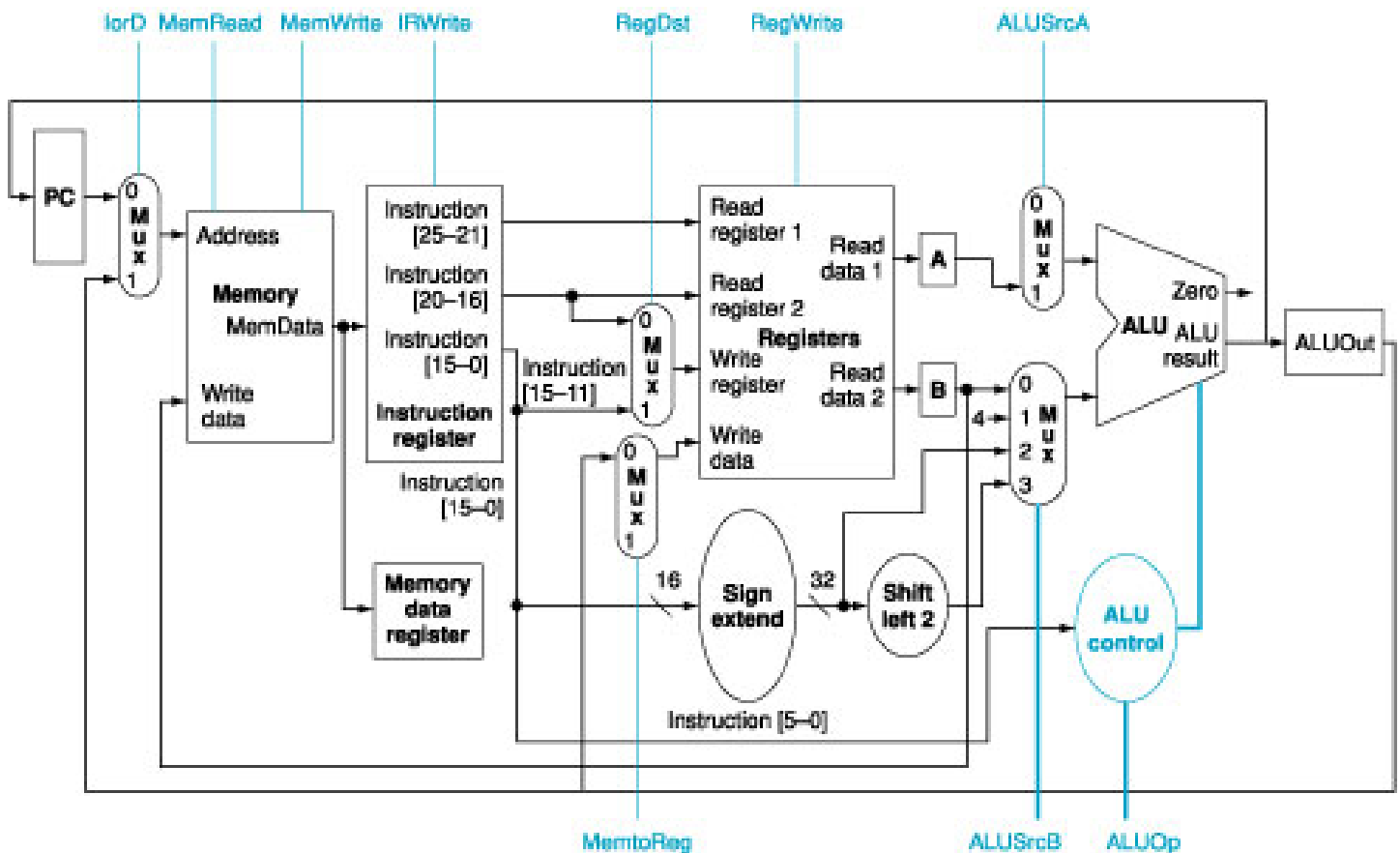


Microprogram-based Control


Control is the hard part of processor design

- Datapath is fairly regular and well-organized
- Memory is highly regular
- Control is irregular and global


Sequencer-based Control Unit

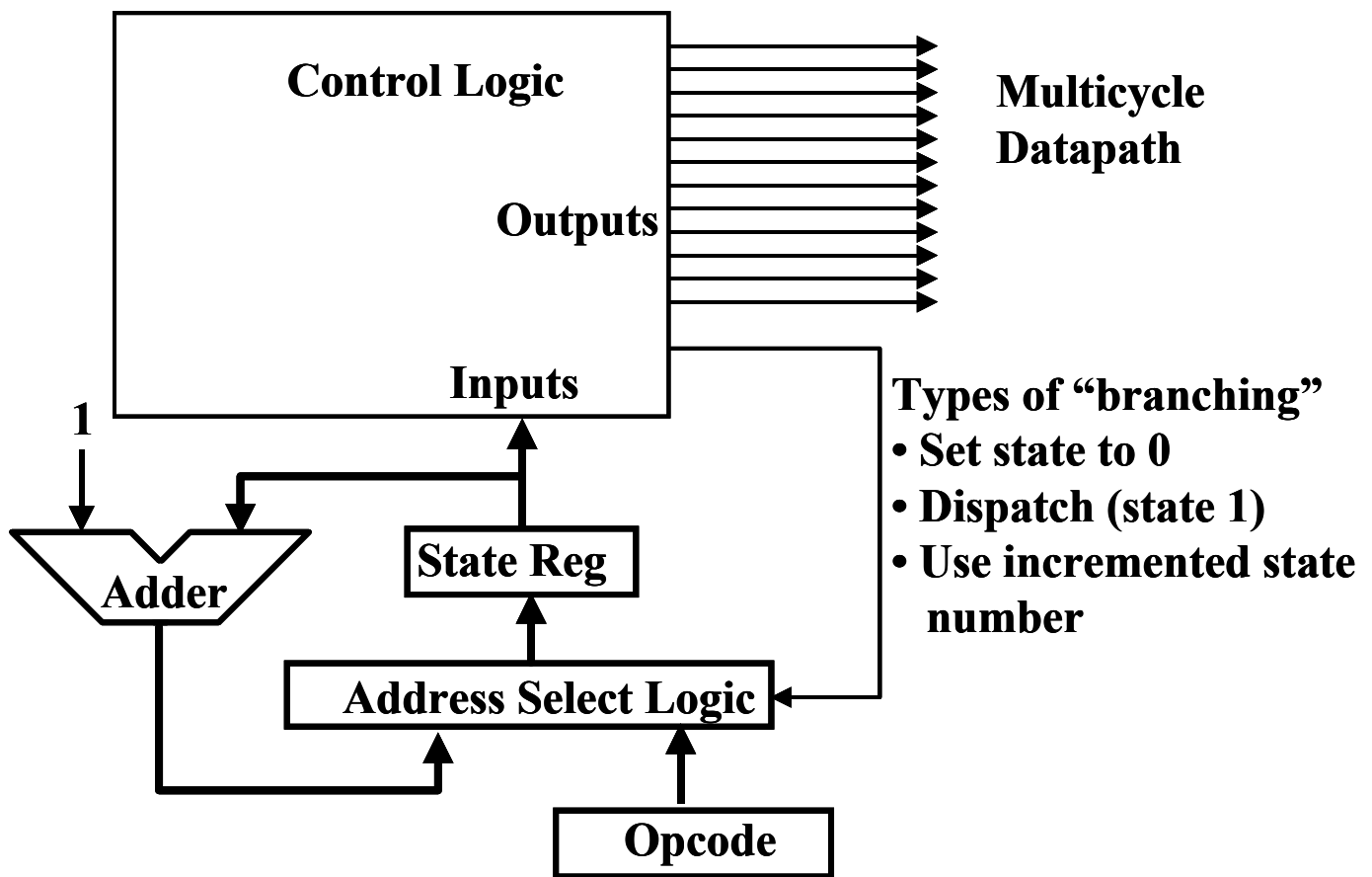


Microprogram-based CPU Control

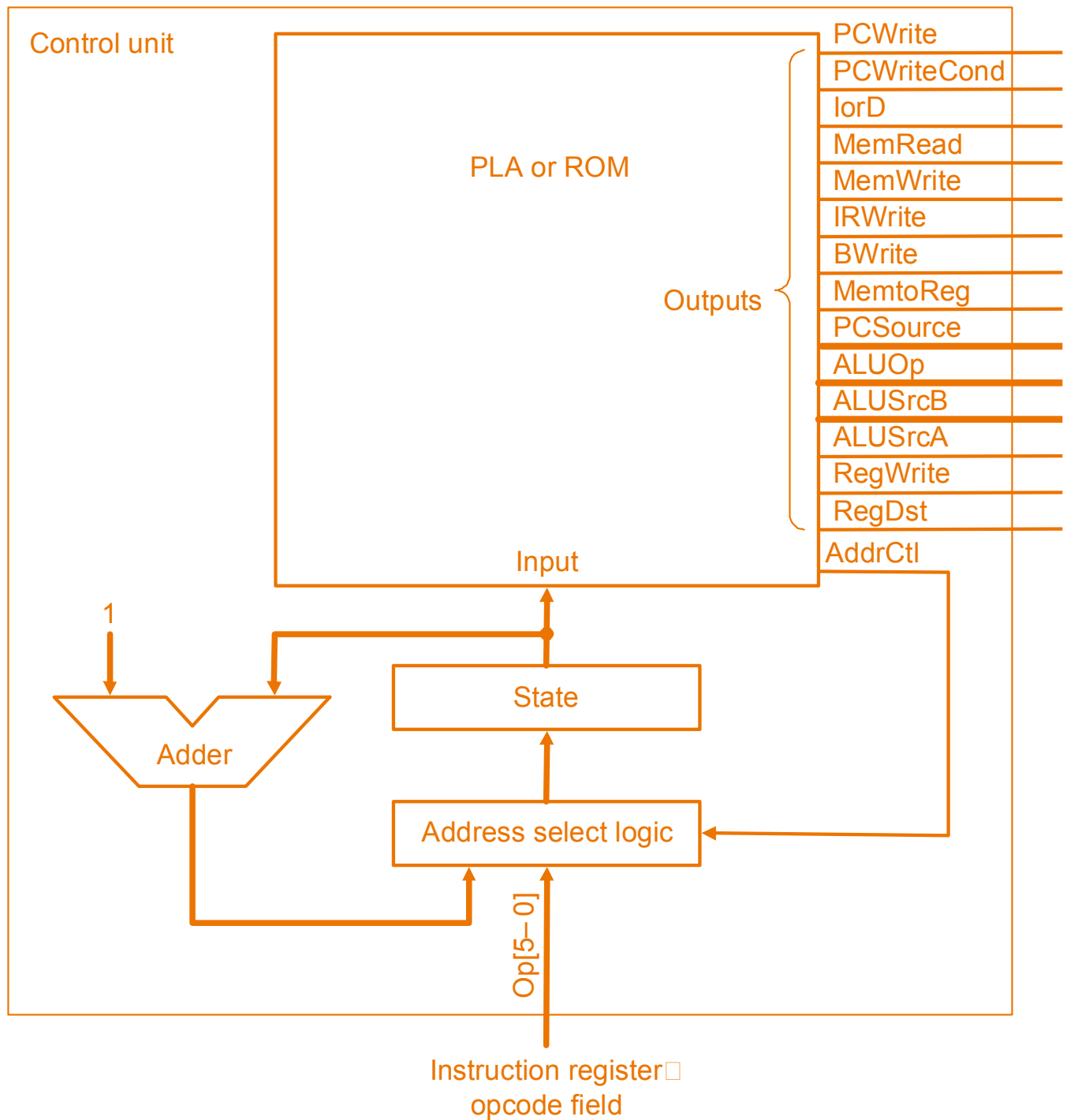

Microprogram-based CPU Control

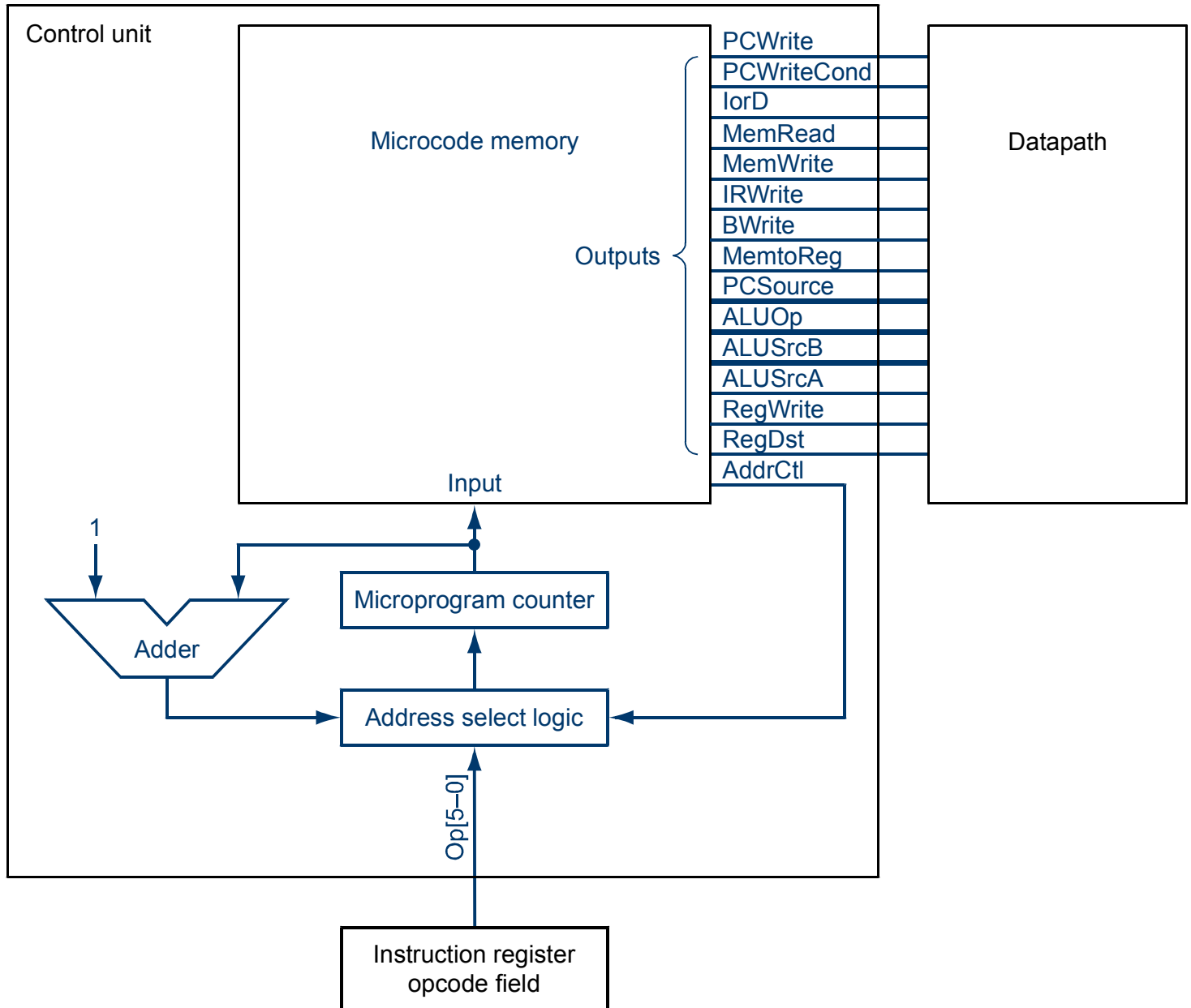

Control Signals

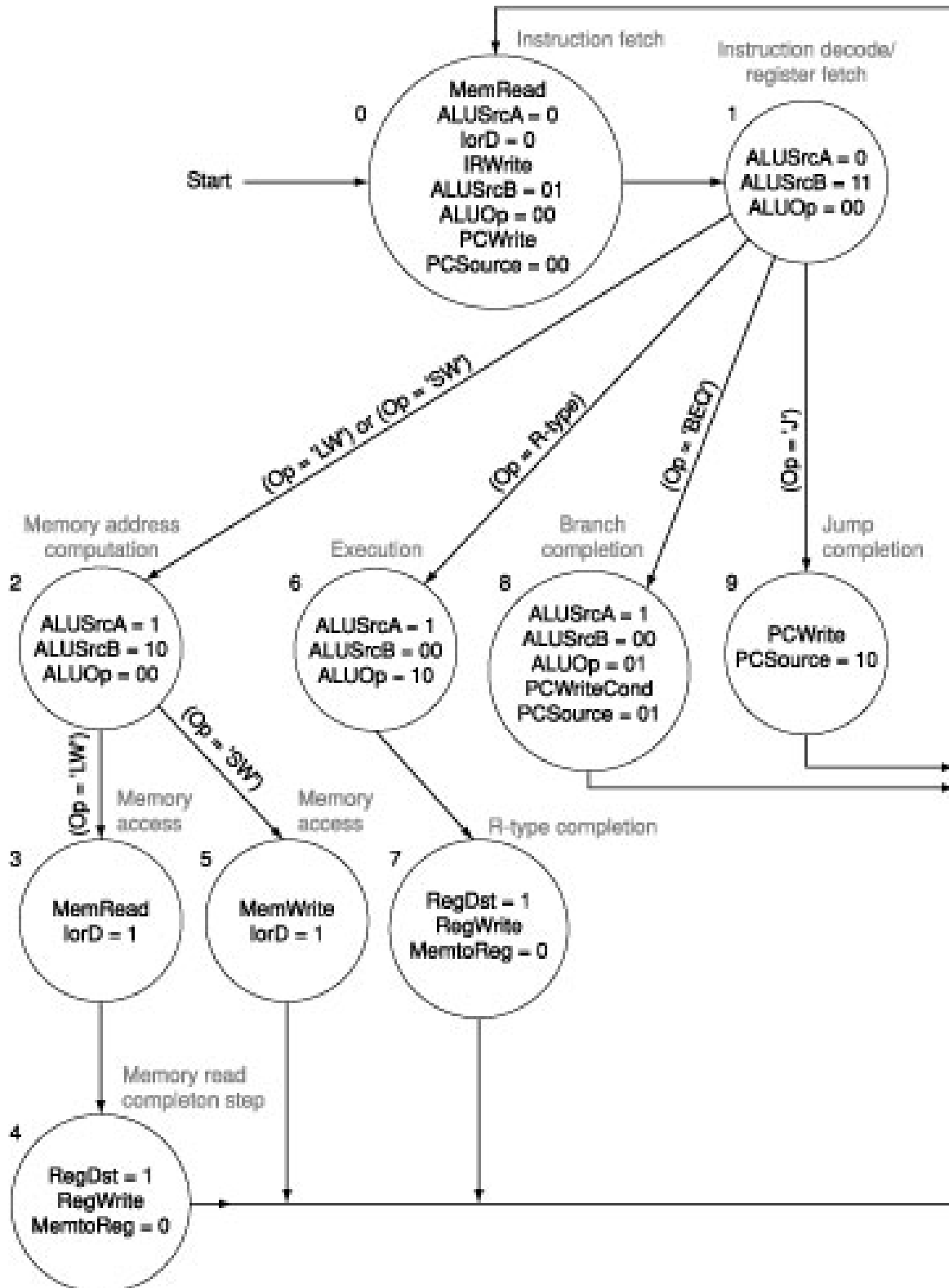


Designing a Microinstruction Set

- Start with list of control signals.
- Group signals together that make sense (vs. random): called “fields”
- Places fields in some logical order (e.g., ALU operation & ALU operands first and microinstruction sequencing last)
- Create a symbolic legend for μ -instruction format, showing name of field values and how they set the control signals
- Use computers to design computers.


μ -assembler to get binary code.

- To minimize the width, encode operations that will never be used at the same time.

Multi-Cycle CPU

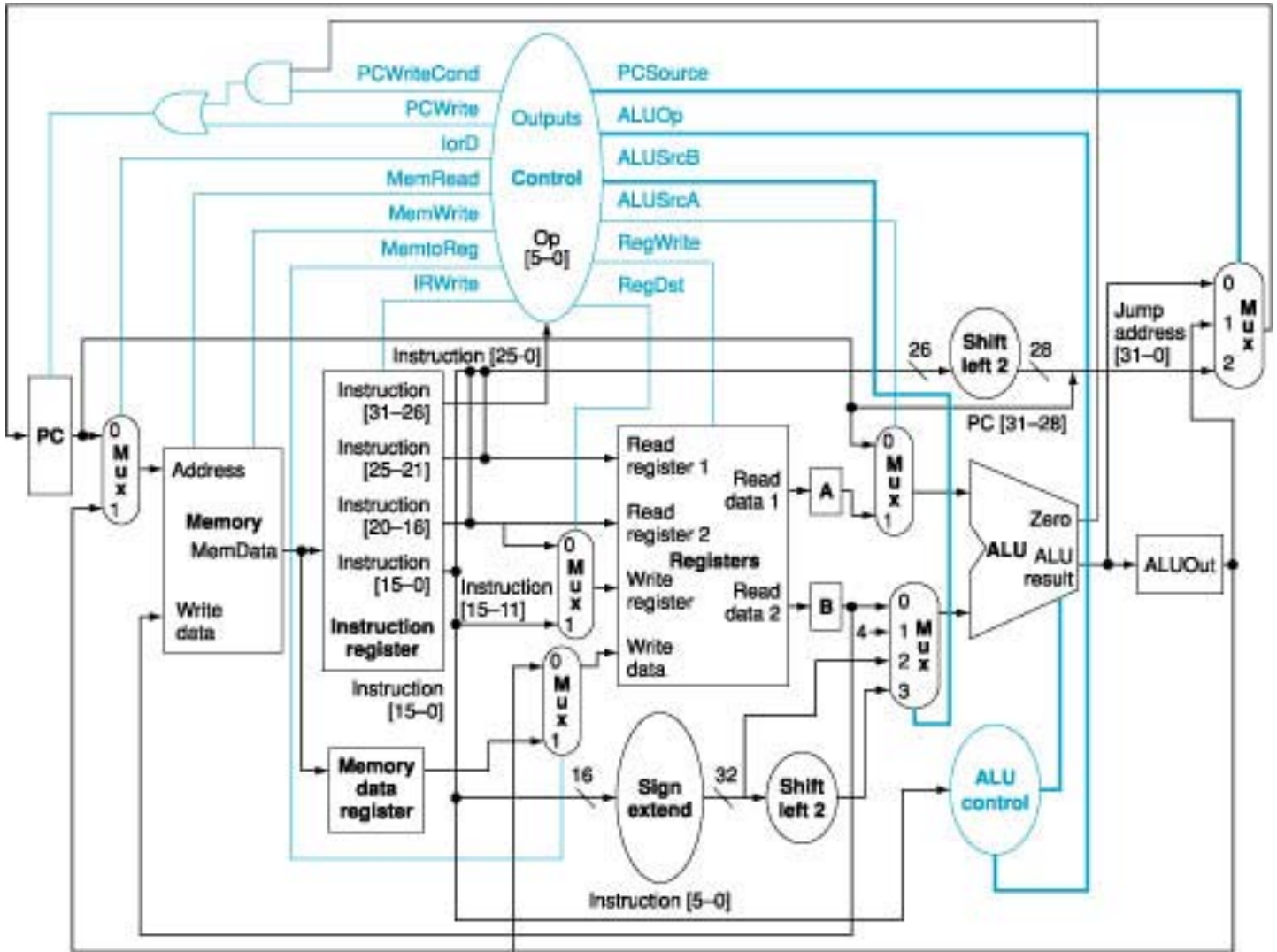

Sequencer-based Control Unit

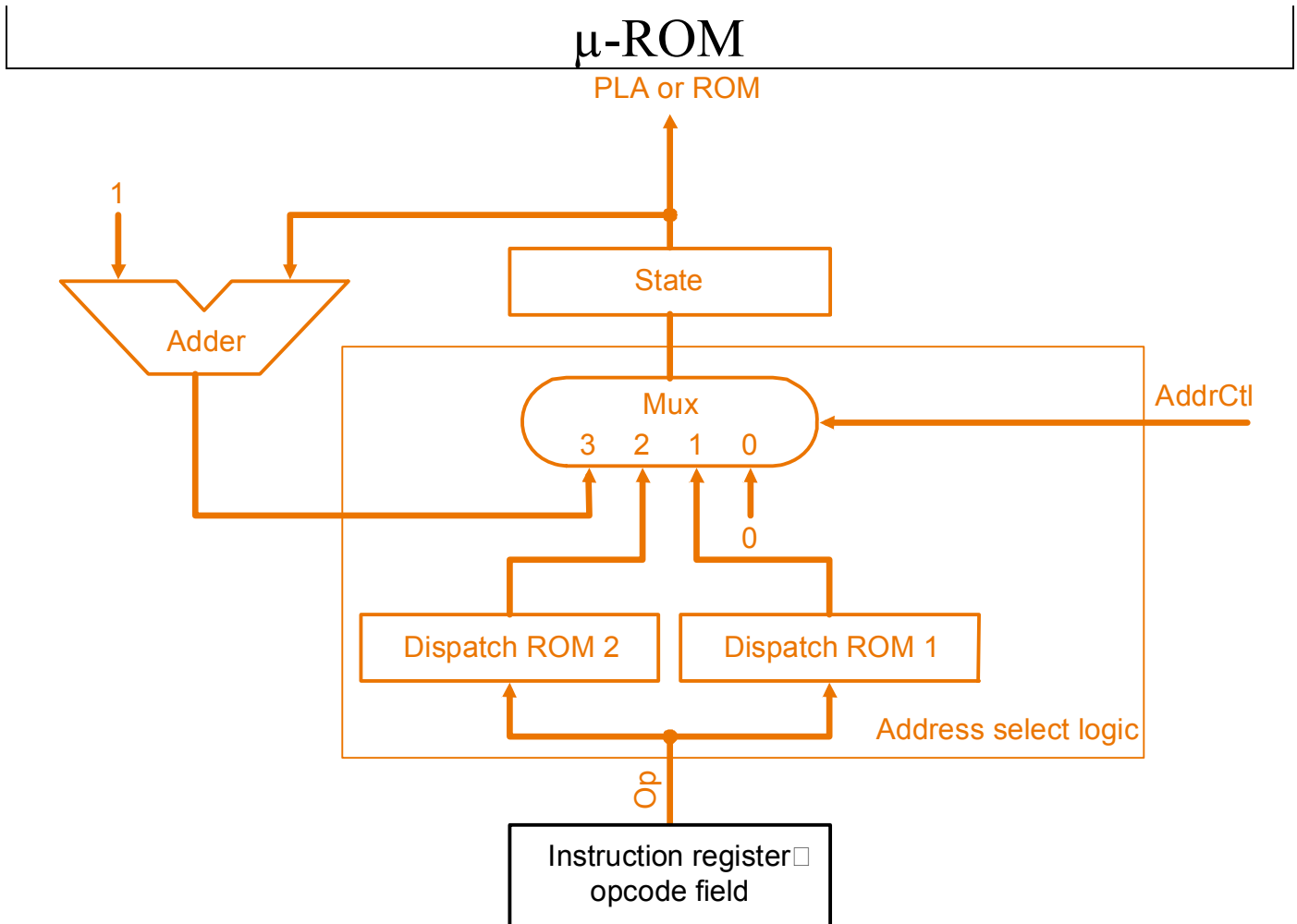

Signal Mux-select _____.

Sequencing	00	Next μ address = 0
	01	Next μ -address = dispatch ROM-1
	10	Next μ -address = dispatch ROM-2
	11	Next μ -address = μ -address + 1

Dispatch ROM 1		
Op	Opcode name	Value
000000	R-format	0110
000010	jmp	1001
000100	beq	1000
100011	lw	0010
101011	sw	0010

Dispatch ROM 2		
Op	Opcode name	Value
100011	lw	0011
101011	sw	0101

μ-instruction Fields & Control Signals

Field name	Value	Signals active	Comment
ALU control	Add	ALUOp = 00	Cause the ALU to add.
	Subt	ALUOp = 01	Cause the ALU to subtract; this implements the compare for branches.
	Func code	ALUOp = 10	Use the instruction's function code to determine ALU control.
SRC1	PC	ALUSrcA = 0	Use the PC as the first ALU input.
	A	ALUSrcA = 1	Register A is the first ALU input.
SRC2	B	ALUSrcB = 00	Register B is the second ALU input.
	4	ALUSrcB = 01	Use 4 as the second ALU input.
	Extend	ALUSrcB = 10	Use output of the sign extension unit as the second ALU input.
	Extshft	ALUSrcB = 11	Use the output of the shift-by-two unit as the second ALU input.
Register control	Read		Read two registers using the rs and rt fields of the IR as the register numbers and putting the data into registers A and B.
	Write ALU	RegWrite, RegDst = 1, MemtoReg = 0	Write a register using the rd field of the IR as the register number and the contents of the ALUOut as the data.
	Write MDR	RegWrite, RegDst = 0, MemtoReg = 1	Write a register using the rt field of the IR as the register number and the contents of the MDR as the data.
Memory	Read PC	MemRead, lorD = 0	Read memory using the PC as address; write result into IR (and the MDR).
	Read ALU	MemRead, lorD = 1	Read memory using the ALUOut as address; write result into MDR.
	Write ALU	MemWrite, lorD = 1	Write memory using the ALUOut as address, contents of B as the data.
PC write control	ALU	PCSource = 00 PCWrite	Write the output of the ALU into the PC.
	ALUOut-cond	PCSource = 01, PCWriteCond	If the Zero output of the ALU is active, write the PC with the contents of the register ALUOut.
	jump address	PCSource = 10, PCWrite	Write the PC with the jump address from the instruction.
Sequencing	Seq	AddrCtl = 11	Choose the next microinstruction sequentially.
	Fetch	AddrCtl = 00	Go to the first microinstruction to begin a new instruction.
	Dispatch 1	AddrCtl = 01	Dispatch using the ROM 1.
	Dispatch 2	AddrCtl = 10	Dispatch using the ROM 2.

ALU Control	SRC1	SRC2	Reg. Control	Memory	PCWrite Control	Sequencing
2-bits	1-bit	2-bits	3-bits	2-bits	4-bits	2-bits

μ-instruction word width = 16-bits

Microprogram Details

Microprogram: Signals specified symbolically

State number	Address-control action	Value of AddrCtl
0	Use incremented state	3
1	Use dispatch ROM 1	1
2	Use dispatch ROM 2	2
3	Use incremented state	3
4	Replace state number by 0	0
5	Replace state number by 0	0
6	Use incremented state	3
7	Replace state number by 0	0
8	Replace state number by 0	0
9	Replace state number by 0	0

Label	ALU control	SRC1	SRC2	Register control	Memory	PCWrite control	Sequencing
Fetch	Add	PC	4		Read PC	ALU	Seq
	Add	PC	Extshft	Read			Dispatch 1
Mem1	Add	A	Extend				Dispatch 2
LW2					Read ALU		Seq
				Write MDR			Fetch
SW2					Write ALU		Fetch
Rformat1	Func code	A	B				Seq
				Write ALU			Fetch
BEQ1	Subt	A	B			ALUOut-cond	Fetch
JUMP1						Jump address	Fetch

R-Format: Fetch, Decode, Rformat1 (ALU), Write-Reg

LW: Fetch, Decode, Mem1 (ALU), Read-Mem, Write-Reg

SW: Fetch, Decode, Mem1 (ALU), SW2 (Write-Mem)

BEQ: Fetch, Decode, BEQ1 (ALU), Update PC

JUMP: Fetch, Decode, Update PC with Jump Address

Micro-Instructions as Store in the ROM

<u>Label</u>	<u>ALU Control</u>	<u>SRC1</u>	<u>SRC2</u>	<u>Reg. Control</u>	<u>Memory</u>	<u>PCWrite Control</u>	<u>Sequencing</u>
<u>ROM Addr</u>	ALU OP 00, 01	ALUSrcA 0, 1	ALUSrcB 00,01,10,11	MemtoReg 0,1 RegDst 0,1 RegWrite	MemRead MemWrite IorD 0,1	PCSource 00,01,10,11 PCWrite,--	Addctl 00,01,10,11
<u>Fetch</u> 0000	00 (add)	0 (PC)	01 (4)	0-RegWrite	0-(IorD) 1(MemRead)	00 1-PCWrite	11 (Seq)
<u>Decode</u> 0001	00 (add)	0 (PC)	11(Extshft)	1- (ld A,B) 0- (RegWrite)	none	none	01 (Dispatch1)
<u>Mem1</u> 0010	00 (add)	1 (A)	10 (Extd)	0- (RegWrite)	none	none	10 (Dispatch2)
<u>LW</u> 0011	none	none	none	none 0-(RegWrite)	1 (IorD) 1(MemRead)	none	11 (Seq)
<u>Reg-Write</u> 0100	none	none	none	1-(RegWrite) 0- (RegDst) 1- MemtoReg	none	none	00 (Fetch)
<u>SW</u> 0101	none	none	none	none 0-(RegWrite)	MemWrite 0(MemRead)	none	00 (Fetch)
<u>RFmt1</u> 0110	10 (Funct-Code)	1 (A)	00 (B)	none 0-(RegWrite)	none	none	11 (Seq)
<u>Reg-Write</u> 0111	none	none	none	1-(RegWrite) 1- (RegDst) 0- MemtoReg	none	none	00 (Fetch)
<u>BEQ</u> 1000	01 (Sub)	1 (A)	00 (B)	none 0-(RegWrite)	none	01-PCSrc PCWrtCond 0-PCWrite	00 (Fetch)
<u>JUMP</u> 1001	00 (add)	0 (PC)	01 (4)	0 (RegWrite)	0 (IorD) 1(MemRead)	10-PCSrc 1-PCWrite	00 (Fetch)

Total of 10 location for μ -Code Memory

Microprogram Details

Micro Instructions for Fetch and Decode

Label	ALU Control	SRC1	SRC2	Reg. Control	Mem	PCWrite Control	Sequence
Fetch	Add	PC	4		Read PC	ALU	Seq
	Add	PC	Ext shift	Read			Dispatch-1

Mem: Fetch Instruction into IR

ALU, SRC1, SRC2: Compute $PC + 4$

PCWrite Control: Write the output of ALU to PC

Sequencing: go to the next microinstruction.

Next Microinstruction is Decode

ALU, SRC1, SRC2: $PC + \text{signext}(\text{IR}[0:15]) \ll 2$

Register Control: Read registers into A and B.

Sequencing: Use dispatch-1 to select one of the following four labels

- ◆ Mem1
- ◆ Rformat1
- ◆ BEQ1
- ◆ JUMP1