

Register Transfer and Datapath Structures

COE608: Computer Organization and Architecture

Dr. Gul N. Khan

<http://www.ee.ryerson.ca/~gnkhan>

Electrical and Computer Engineering

Ryerson University

Overview

- Introduction to Register Transfer
- Design of Datapaths and Processor Control
- Datapath Representation
- Datapath Interconnection Strategies and Register Transfer Operations
 - ◆ Point-to-Point Transfer
 - ◆ Bus-based Transfer
 - ◆ Multiple Busses
- Typical ALU-Datapath Diagrams

Chapter 4 of the text book

Chapter 7 “Logic and Computer Design” by Mano & Kime


Motivation

Computer Design Example: By Using Combinational and Sequential Logic Circuit Design Procedure.

- **Computer**
- **Processing Unit**
- **Control** = Finite State Machine
 - ◆ Inputs
 - ◆ Outputs
 - ◆ Instruction Interpretation = Instruction Fetch, Decode, Execute
- **Datapath**
 - ◆ Functional Units = ALU, Multipliers, Dividers, etc.
 - ◆ Registers = Program Counter, Shifters, Storage Registers

In addition to registers, datapath contains the digital logic consisting of buses, MUXes, decoders and processing circuits.

Structure of a Computer

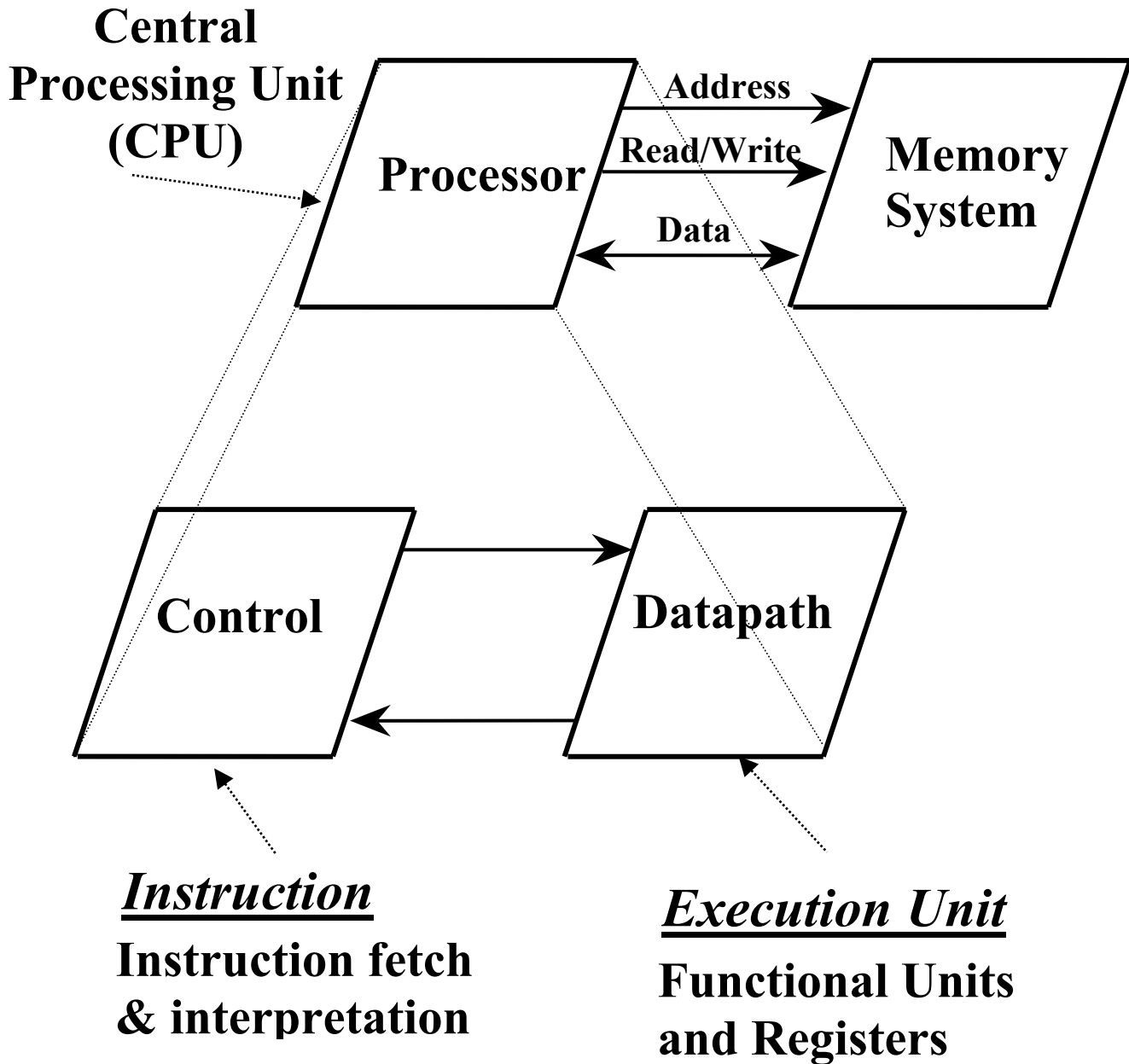

Instruction Sequencing

Example Instruction: Add R_X to R_Y and place result in R_Z .

- **Fetch:** Get the Add instruction from memory to Instruction Register (IR)
- **Decode Instruction**
 - ◆ Instruction in IR is an ADD
 - ◆ Source operands are in R_X , R_Y
 - ◆ Destination operand is in R_Z
- **Execute Instruction**
 - ◆ Move R_X , R_Y to ALU
 - ◆ Set up ALU to perform ADD function
 - ◆ ADD R_X to R_Y
 - ◆ Move ALU result to R_Z


Instruction Types

- **Data Manipulation**
Add, Subtract, etc.
- **Data Staging**
Load/Store data to/from memory
Register-to-register move
- **Control**
Conditional/unconditional branches.
Subroutine calls and returns.

Control Unit

Elements of the Control Unit

Finite State Machine Elements:

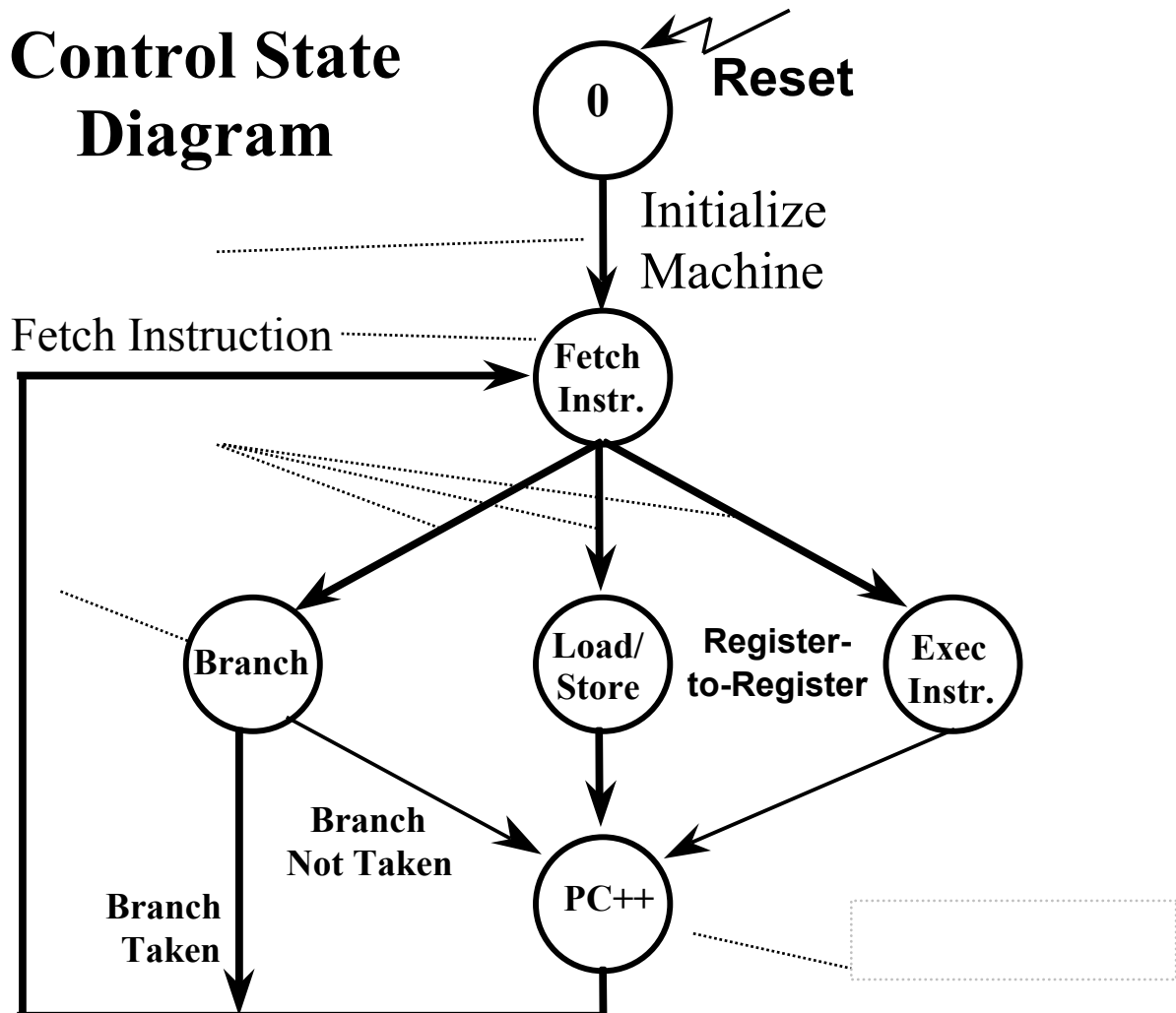


RT: Register Transfer

Data transfer from one register to another is represented in symbolic form as:


$R2 \leftarrow R1$;

Source Register: R1

Destination Register: R2

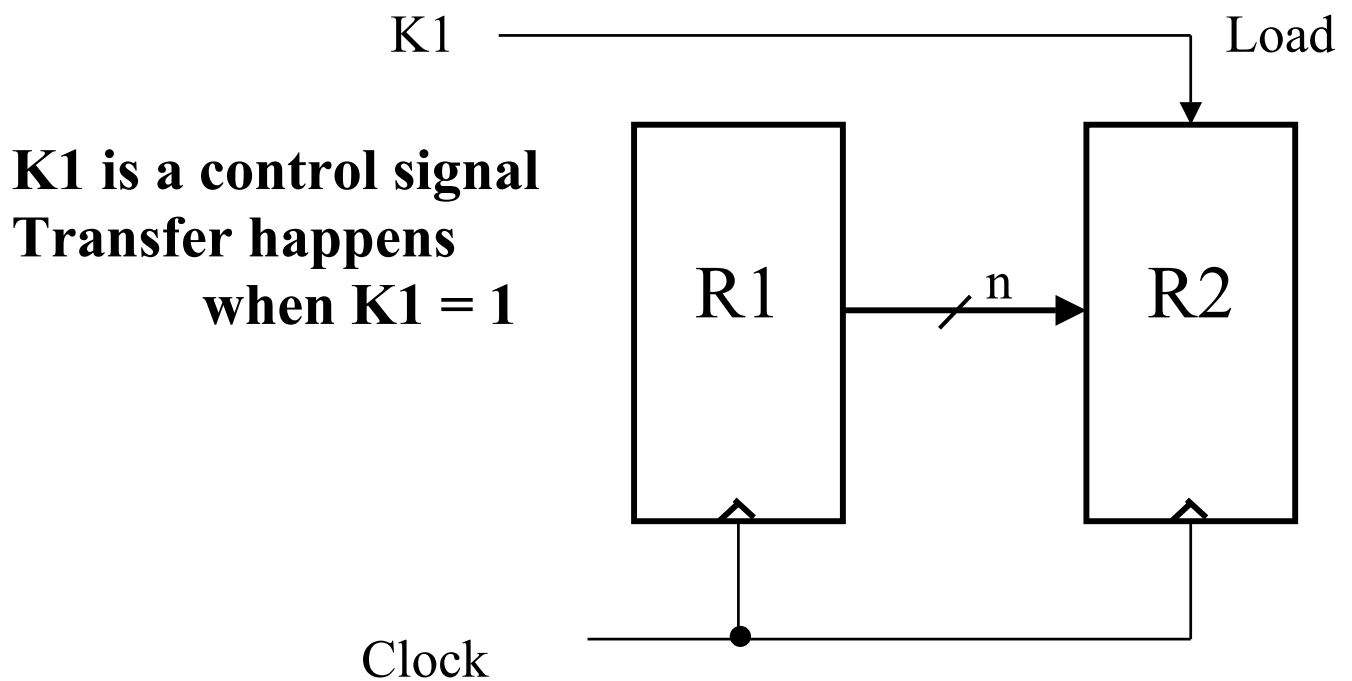

 If $(K1=1)$ then $(R2 \leftarrow R1)$ or $K1: R2 \leftarrow R1$



Register Transfer

Basic Symbols for RT Operations

Symbol	Description	Examples
Letters and numerals	Denotes a register	AR, R2, DR, IR, PC
Parentheses	Denotes a part of the register	R2(1), R2(7:0)
Arrow	Denotes transfer of data	R2 \leftarrow R1
Comma	Separate and simultaneous transfers	R2 \leftarrow R1, R0 \leftarrow R1, R4 \leftarrow R3
Square Brackets	Specifies an address for memory	DR \leftarrow M[ADR]

RT: Register Transfer

Trace an Instruction

$AC \leftarrow AC + Mem\langle address \rangle$

1) Instruction Fetch

- Move PC to MAR
- Initiate a memory read sequence
- Move data from memory to IR

2) Instruction Decode

- Op code bits of IR are input to control FSM
- Rest of the IR bits encode the operand address

3) Operand Fetch

- Move operand address from IR to MAR
- Initiate a memory read sequence

4) Instruction Execute

- Data available on load path
- Move data to ALU input
- Configure ALU to perform ADD operation
- Move S result to AC

5) House-keeping

- Increment PC to point at next instruction

Register Transfer

Control Unit generates control signals

- to transfer data from one register to another.

Register Transfer and Micro-Operations

Instruction Fetch:

MAR \leftarrow PC ;
Memory Read;
IR \leftarrow Memory;

Instruction Decode:

IF IR<op code> = ADD_FROM_MEMORY THEN

Instruction Execution:

MAR \leftarrow IR<addr>;
Memory Read;
ALU B \leftarrow Memory;
ALU A \leftarrow AC ;
ALU ADD;
AC \leftarrow ALU S;

Assert Control Signal for

PC \leftarrow PC+1;

Micro-Operations

Micro-operations are the elementary operations performed on Registers.

- Usually performed in one clock cycle.
 - Multiple (independent) micro-operations can be performed in one clock cycle.
 - One micro-operation for each control point.
- ✓ Control units provide control signals to sequence micro-operations in a prescribed manner.
- ✓ RT operations can be decomposed into one or more micro-operations.

Register Transfer

$AC_1 \leftarrow AC_1 + AC_2$

Micro-operations

$PC \leftarrow 0$

$PC \leftarrow PC+1$

Address Bus \leftarrow MAR

$0 \rightarrow PC$

$PC+1 \rightarrow PC$

MAR \rightarrow Address Bus

Datapath Interconnection Strategies

Tradeoffs between datapath/control complexity and amount of parallelism supported by hardware.

How to interconnect hardware resources of the datapath?

Case Study:

Consider 4 general-purpose registers that must be able to exchange their contents.

- Methods of interconnection.
- Datapath support for register-to-register swap.

RT notation for swap instruction

SWAP(R_i, R_j)

Register-to-Register Communication

Point-to-Point Connection


MUX Based Data Transfer

If $(K1 = 1)$ then $(R0 \leftarrow R1)$ else

If $(K2 = 1)$ then $(R0 \leftarrow R2)$

$K1$ and $K2$ control signals that control RT as:

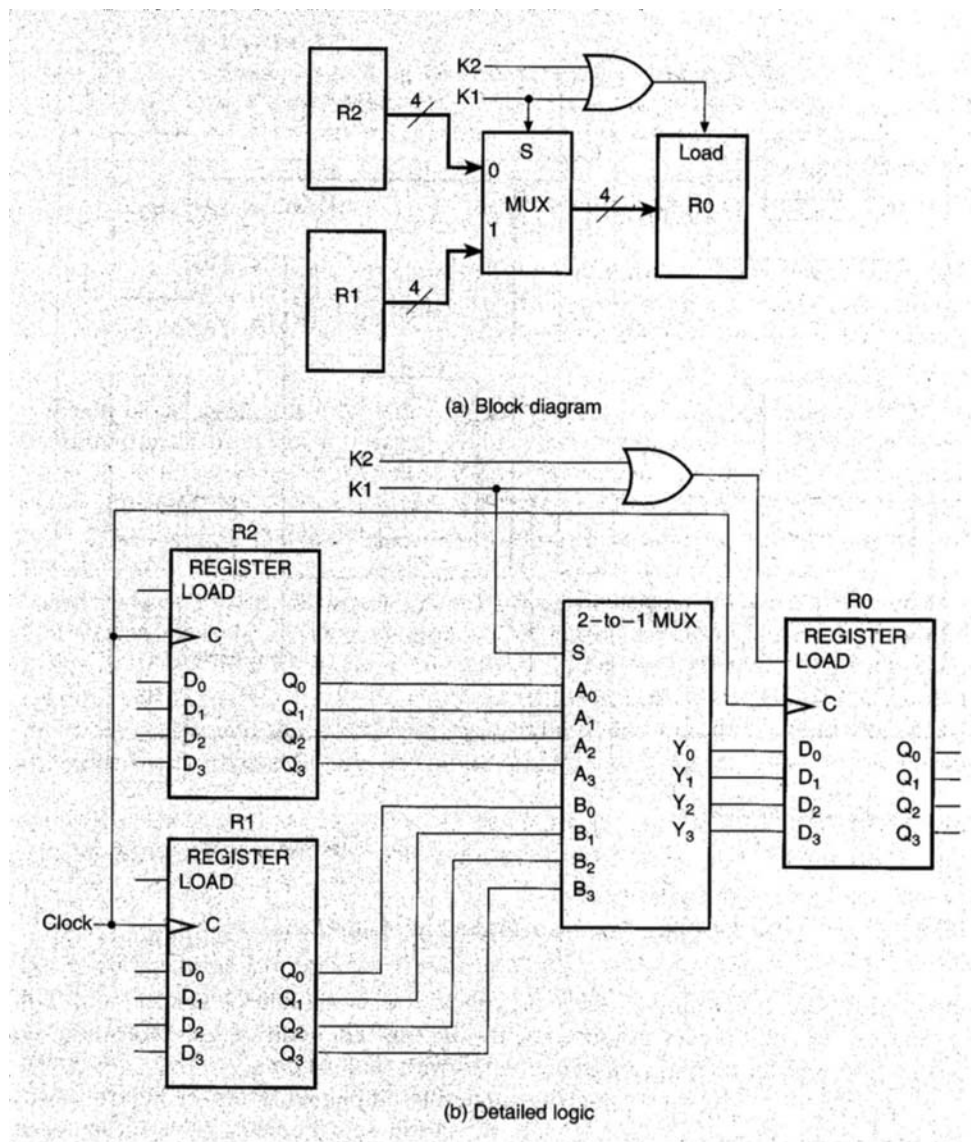
$K1: R0 \leftarrow R1, \quad K1K2: R0 \leftarrow R2$



- Dedicated paths need large amount of logic.
- Excessive number of interconnections.

Point-to-Point Connection

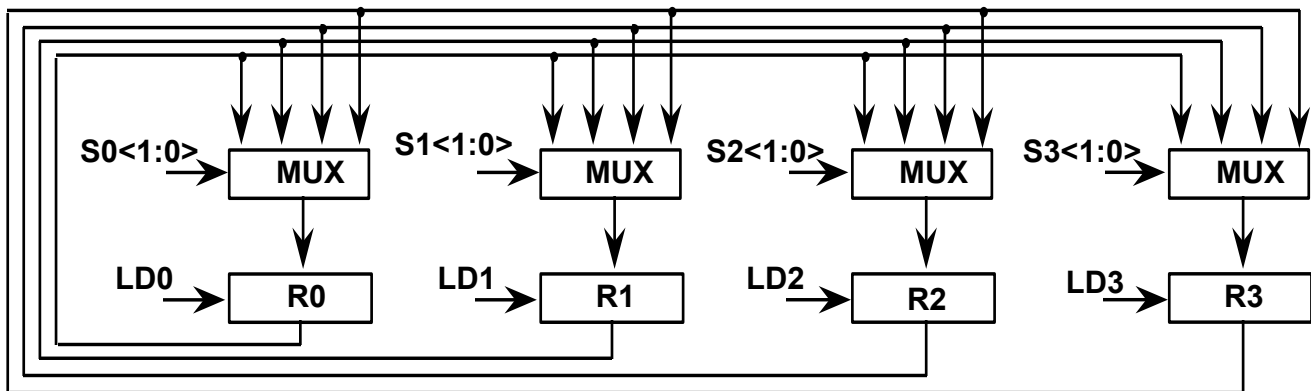Four registers interconnected via 4:1 MUXEs and point-to-point connections



Edge-triggered N-bit registers controlled by LD_i control signals

N x 4:1 Multiplexers per register that are controlled by S_i<1:0> control signals.

Control of Register SWAP Operation

SWAP(R1, R2) Control Signals

01 → S2<1:0>;

10 → S1<1:0>;

1 → LD2;

1 → LD1;

Point-to-Point Connections

Multiple Register Transfers:

$R0 \leftarrow R1$ and $R3 \leftarrow R2$


01 \rightarrow S0<1:0>;

10 \rightarrow S3<1:0>;

1 \rightarrow LD0;

1 \rightarrow LD3;

Control Signals Assertion

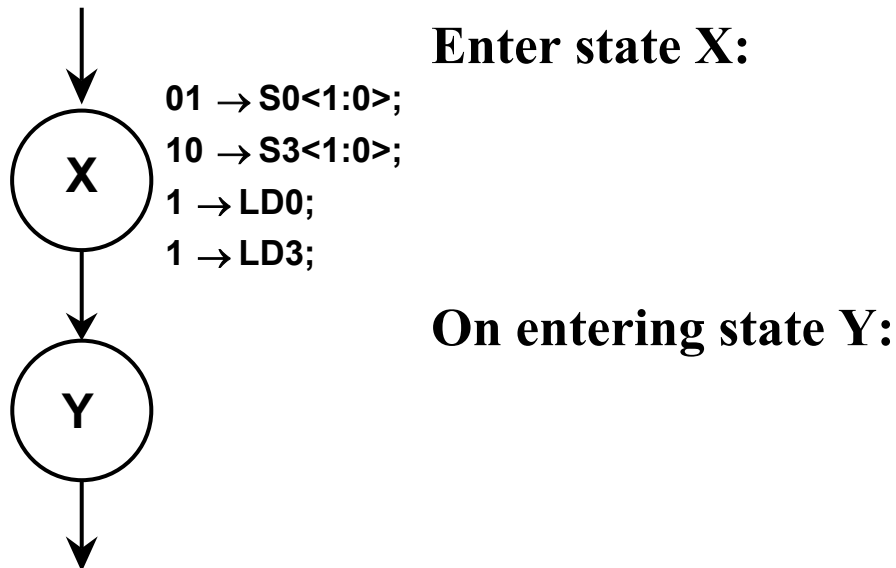

Advantages and Disadvantages

Bus-Based Transfer

Bus is a set of common lines driven by selection logic.


- Bus-based transfer is an efficient scheme that uses shared transfer path.
- Control signals select a single source and one or multiple destinations on a clock cycle for which the transfer takes place.

Transfers between 3-Registers

Dedicated Multiplexers

Single Bus System


MUX and Bus Transfer

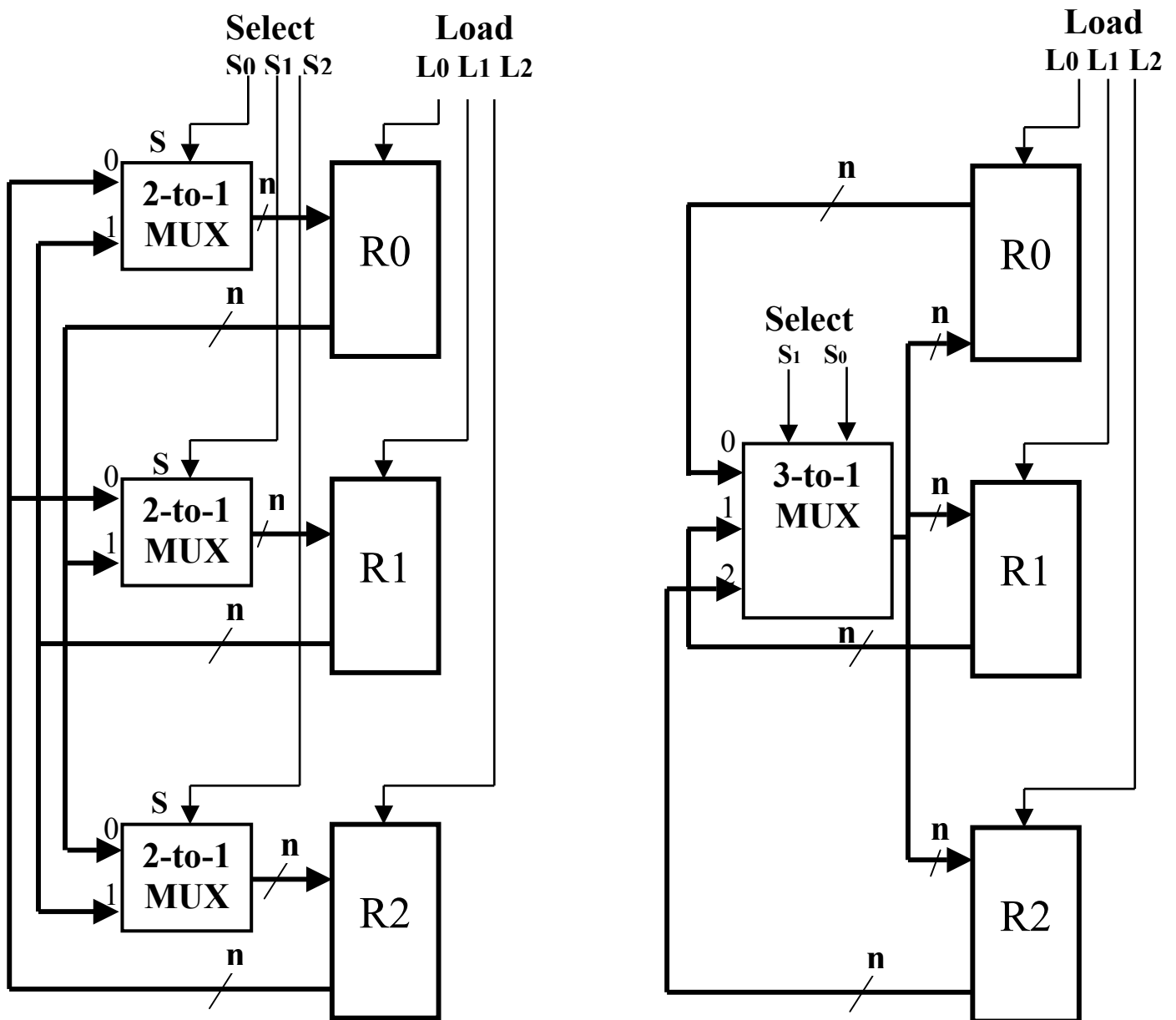

Single Bus Register Transfers

Register Transfer	CONTROL SIGNALS				
	Select		Load		
	S1	S0	L2	L1	L0
$R0 \leftarrow R2$					
$R0 \leftarrow R1, R2 \leftarrow R1$					
$R0 \leftarrow R1, R1 \leftarrow R0$					

Single Bus Interconnection

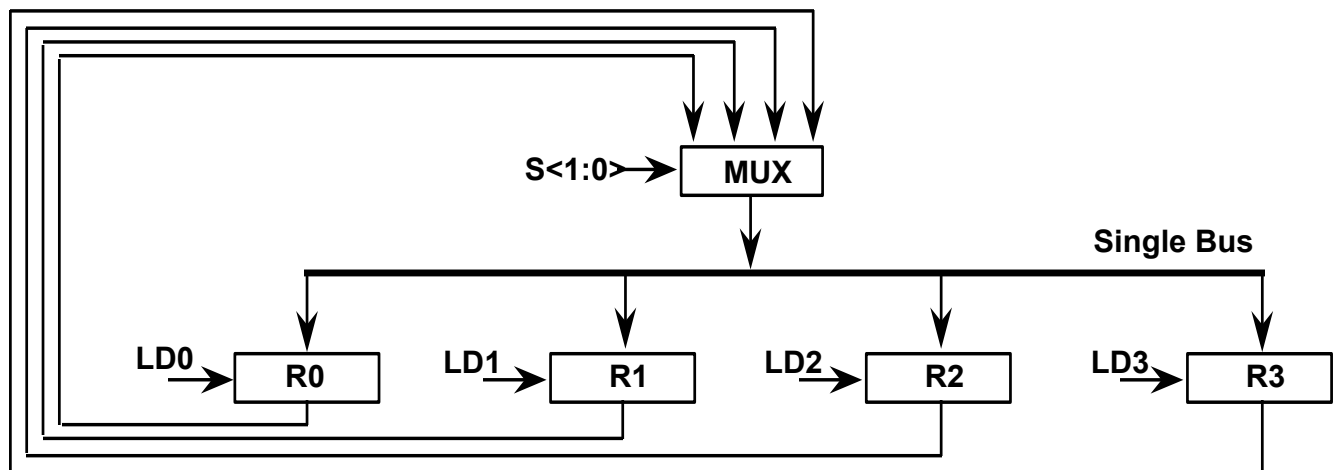

- Register MUX blocks replaced by a single block.
- 25% hardware cost of the previous alternative.
- Shared set of pathways is called a BUS.

RT Operations **$R0 \leftarrow R1$ and $R3 \leftarrow R2$**

State X: **$(R0 \leftarrow R1)$**
01 \rightarrow **$S\langle 1:0 \rangle$** ;
1 \rightarrow **$LD0$** ;

State Y: **$(R3 \leftarrow R2)$**
10 \rightarrow **$S\langle 1:0 \rangle$** ;
1 \rightarrow **$LD3$** ;

Datapath no longer supports two simultaneous transfers!
Two control states are required for transfers.

Single Bus Interconnection

SWAP Operation

- A special TEMP register must be introduced ("Register 4")

State X: $(R4 \leftarrow R1)$

Control Signals

Three states are required rather than one! plus extra register and wider MUX

State Y: $(R1 \leftarrow R2)$

Control Signals


More control states because this datapath supports less parallel activity

State Z: $(R2 \leftarrow R4)$

Engineering choices made based on how frequently multiple transfers take place at the same time


Alternatives to Multiplexers

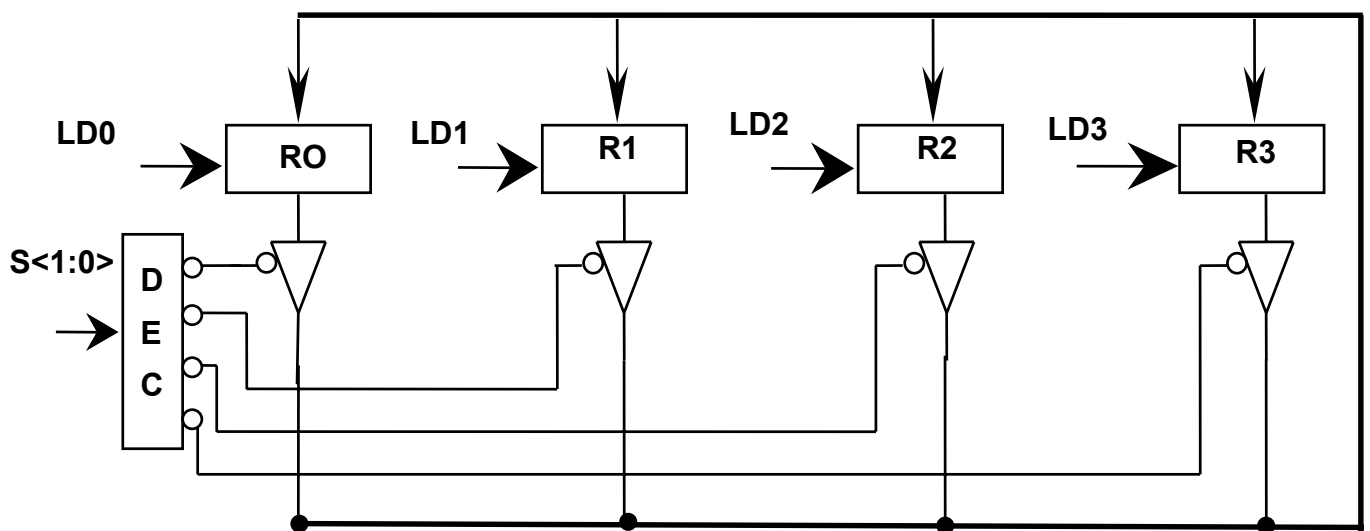Tri-state buffers as an interconnection scheme



Decoder decodes the input control lines $S\langle 1:0 \rangle$ and generates one select signal to enable only one tri-state buffer.

Three-State Bus

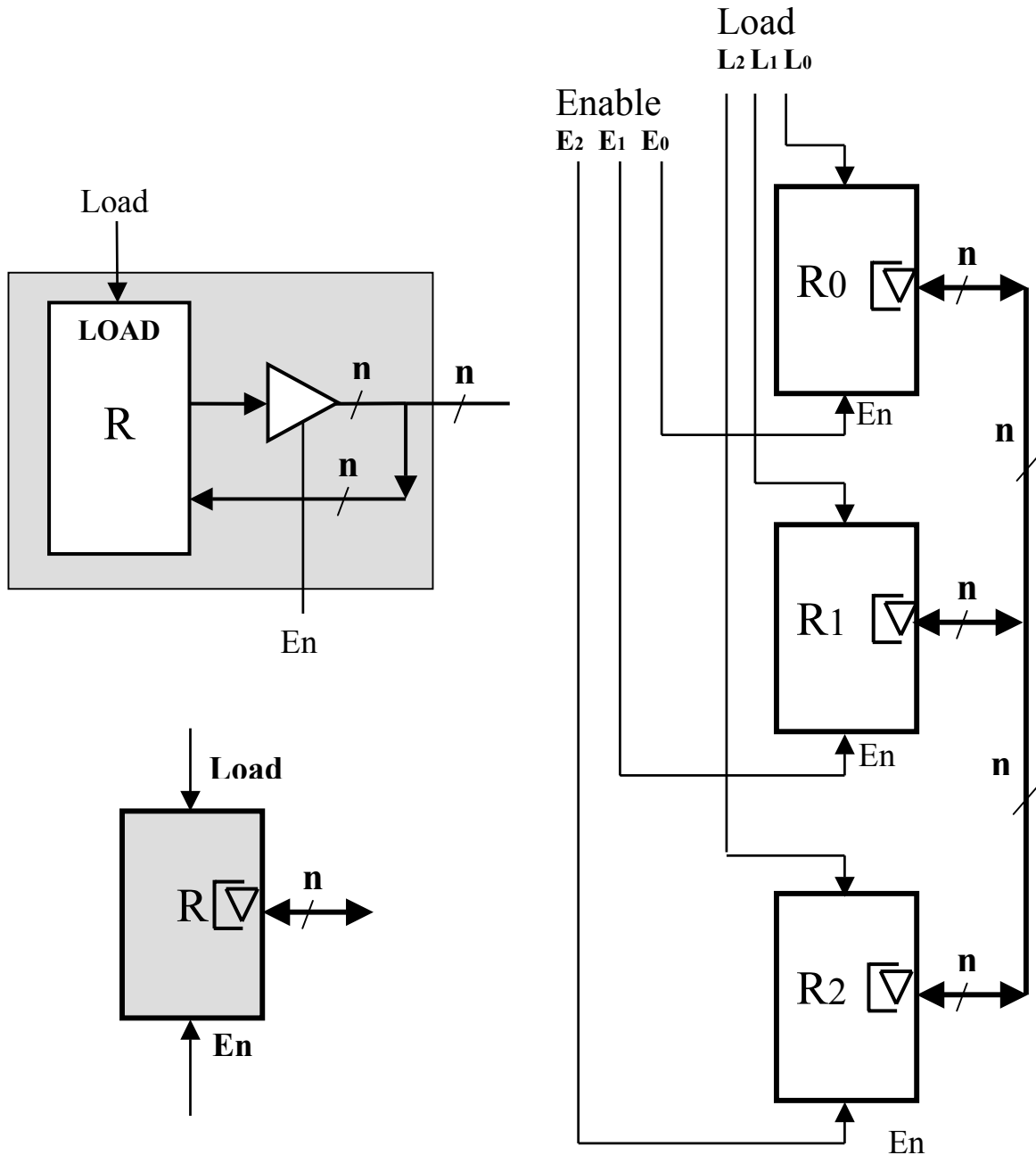

Three-state bus using registers with bi-directional lines


Three-State Bus

Three-state buffer based bus has the potential of reduction in the number of connections.

Many 3-state buffer outputs can be connected together to form one-bit line of a bus.

Main Advantages:

 - 3-state based bus has one level of logic gates as compared to MUX that may require multiple-level OR gates due to limited fan-in.
- 3-state buffers provide fast buses with multiple sources.
- Reduced (half) data connections to the set of register blocks for each bit of the bus.




3-state buses are suitable for interconnection between different physical packages.

Bus-based Interconnection

Real datapaths are a compromise between extremes.

Register Transfer Diagram

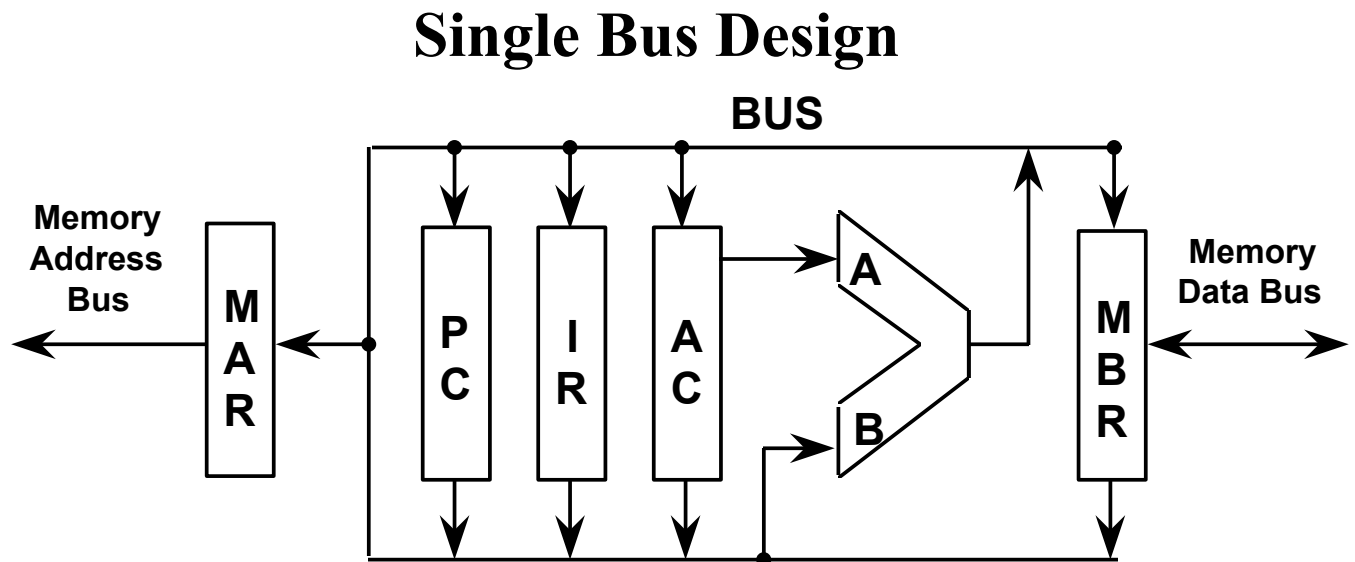

Register Transfer Operations

BUS <= PC

BUS <= IR

BUS <= AC

BUS <= MBR

BUS <= ALU Result

PC <= BUS

IR <= BUS

AC <= BUS

MBR <= BUS

ALU B <= BUS

MAR <= BUS

ALU <= AC

("hardwired")

Single Bus

Example:

Register Transfer for Single Bus Design

Instruction Interpretation for "ADD Mem[X]"

Fetch Operand

Cycle 1: BUS \leftarrow IR<operand address> ;
 MAR \leftarrow BUS ;

Cycle 2: Memory Read;
 MBR \leftarrow Databus ;


Perform ADD

Cycle 3: BUS \leftarrow MBR ;
 ALU B \leftarrow BUS ;
 ALU A \leftarrow AC ;
 ADD;

Write Result BUS \leftarrow ALU Result ;
 AC \leftarrow BUS ;

Multiple Buses

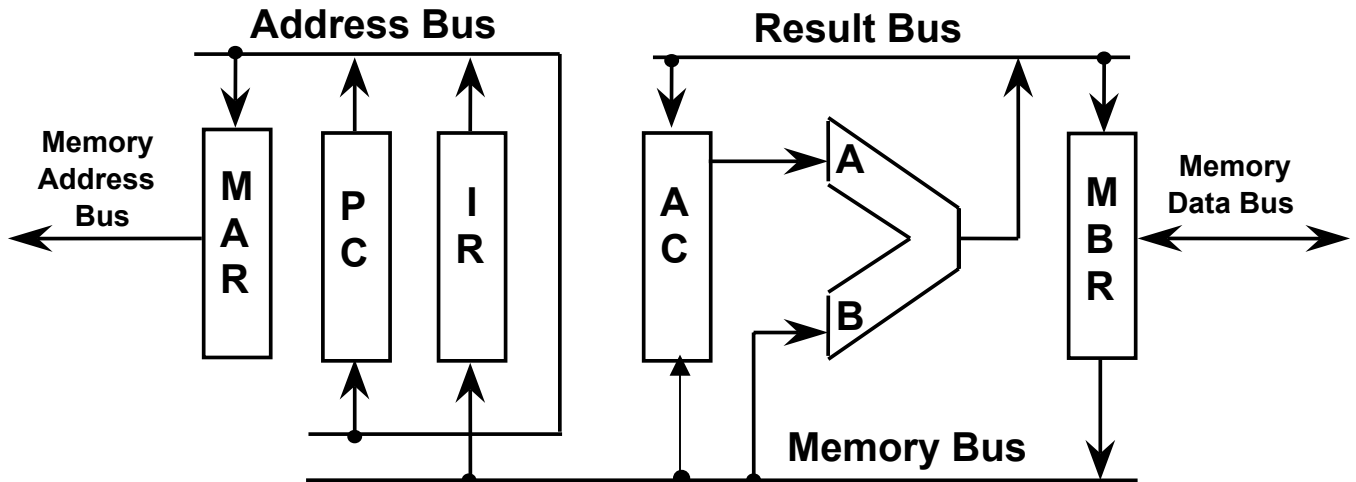Three Bus Design - Supports more Parallelism



Single bus replaced by three buses:

- MBUS: Memory Bus
- RBUS: Result Bus
- ABUS: Address Bus

Instruction Interpretation for "ADD Mem[X]"

Fetch Operand

Cycle 1: ABUS \leftarrow IR<operand address>;
MAR \leftarrow ABUS;

Cycle 2: Memory Read;
MBR \leftarrow Databus;


Perform ADD

Cycle 3: MBUS \leftarrow MBR;
ALU B \leftarrow MBUS;
ALU A \leftarrow AC;
ADD;

Write Result

RBUS \leftarrow ALU Result;
AC \leftarrow RBUS ;

ALU

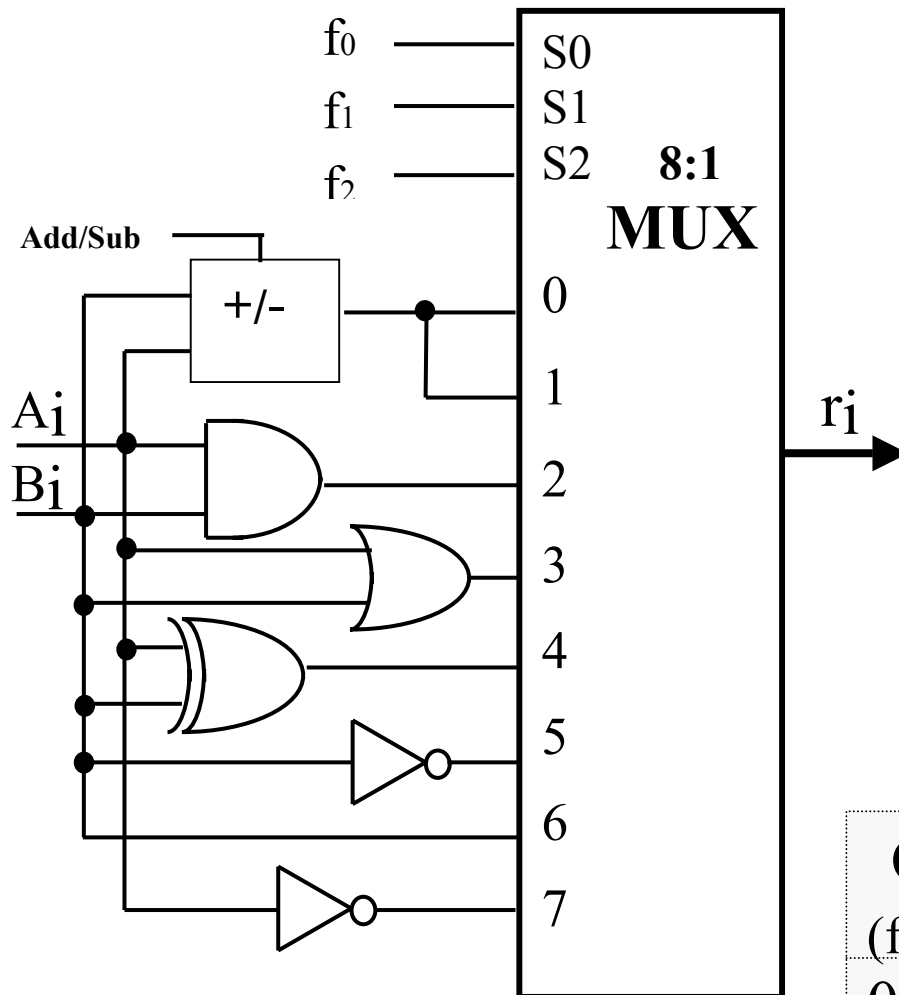

Add/Sub = f_0

Op ($f_2 f_1 f_0$)	Result, r_i
000	$A_i + B_i$
001	$A_i - B_i$
010	$A_i \cdot B_i$
011	$A_i \parallel B_i$
100	$A_i \oplus B_i$
101	$\overline{A_i}$
110	A_i
111	$\overline{B_i}$

32-bit ALU (VHDL Code)

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
entity alu is
  port(
    A,B : in std_logic_vector(31 downto 0);
    OP  : in std_logic_vector(2 downto 0);
    Ri  : out std_logic_vector(31 downto 0));
end alu;
architecture alu of alu is
  signal tmp : std_logic_vector(31 downto 0);
begin
  process(OP, A, B)
  begin
    case OP is
      when "000" => tmp <= A + B;
      when "001" => tmp <= A - B;
      when "010" => tmp <= A and B;
      when "011" => tmp(31 downto 0) <= A or B ;
      when "100" => tmp <= A xor B ;
      when "101" => tmp <= not A ;
      when "110" => tmp <= A ;
      when "111" => tmp <= not B ;
      when others => tmp <= "00000000000000000000000000000000";
    end case;
    Ri <= tmp ;
  end process;
end alu;
```

Datapath

Block diagram of a datapath containing registers, buses, MUXes, decoders and processing units.

