

Computer Arithmetic

COE608: Computer Organization and Architecture

Dr. Gul N. Khan

<http://www.ee.ryerson.ca/~gnkhan>

Electrical and Computer Engineering

Ryerson University

Overview

- Computer Arithmetic: Overview
 - ◆ 2's complement numbers
 - ◆ Addition, Subtraction and Logical Operations
- Constructing an Arithmetic Logic Unit
- Multiplication and Division
- Floating Point Arithmetic

Chapter 3 of the text

Digital Arithmetic

Arithmetic operations in digital computers are performed on binary numbers.

Main Arithmetic Operations

- Addition, Subtraction, Multiplication, Division

Binary Addition

Operand-1	Operand-2	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


$$\begin{array}{r} 10110 \\ + 00111 \\ \hline \end{array} \quad \begin{array}{r} 11.101 \\ + 10.011 \\ \hline \end{array}$$

Sign-Magnitude System

Magnitude and Sign is represented distinctively.

For an eight-bit signed number

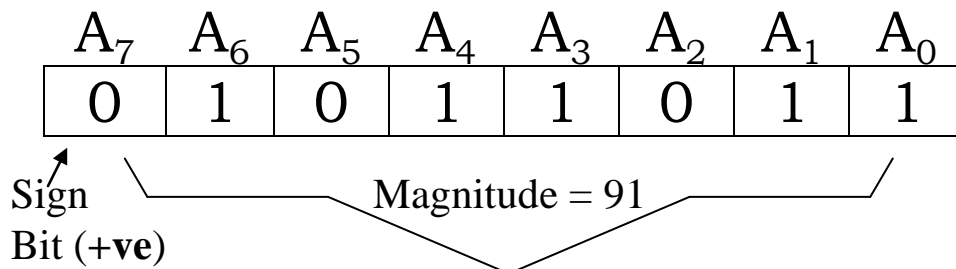- MSB represents sign of the number.
- 7-bits represent magnitude ≤ 127 .



2's Complement System

Sign-Magnitude based arithmetic is hard to implement in hardware

2's complement system is mostly used for signed binary numbers

1's Complement

2's Complement

(22)	10110
1's complement	
<hr/>	

Negation

Converting a +ve number to its -ve equivalent or a -ve number to its +ve equivalent

➤ *2's complement* conversion is only needed for -ve numbers

2's Complement Representation

Positive Number

Add a sign bit '0' in front of the MSB

Negative Number

1. Obtain the binary representation of the magnitude of number
2. Obtain 2's complement of the magnitude
3. Add a sign bit 1 (for -ve number) in front of the MSB of the 2's complement obtained in step 2.

A short cut method

Begin from LSB and move left bit-by-bit towards the MSB.

- i) If the bit is 0, simply copy down the bit.
- ii) Repeat step i) until the first bit of 1 is encountered, now copy down this bit.
- iii) For all subsequent bits, simply invert each one of them.

Example: 2's complement of -42

Decimal Values of 2's Complement

Positive Numbers

- MSB is the sign bit = 0
 - decimal value equals to binary equivalent
- 2's complement of 0 10010 = 18

Negative Numbers

- sign bit is 1
- obtain 2's complement of N-bit magnitude part
- decimal value is equal to -ve of the 2's complement

Decimal value of 1 01110 ?

Sign bit = 1

2's complement of 01110

2's complement number 1 01110 = -18

Special Case

When sign bit = 1 and all other bits equal zero
decimal value of the 2's complement = -2^N

e.g. 1 00000

Addition in 2's Complement System

Addition of two positive numbers

$$\begin{array}{r} +9 \quad 0 \ 1 \ 0 \ 0 \ 1 \\ +4 \quad 0 \ 0 \ 1 \ 0 \ 0 \\ \hline \end{array}$$

Addition of +ve and smaller -ve number

$$\begin{array}{r} +9 \quad 0 \ 1 \ 0 \ 0 \ 1 \\ -4 \quad 1 \ 1 \ 1 \ 0 \ 0 \\ \hline \end{array}$$

Addition of a +ve and larger -ve number

$$\begin{array}{r} -9 \quad 1 \ 0 \ 1 \ 1 \ 1 \\ +4 \quad 0 \ 0 \ 1 \ 0 \ 0 \\ \hline \end{array}$$

Addition of two negative numbers

$$\begin{array}{r} -9 \quad 1 \ 0 \ 1 \ 1 \ 1 \\ -4 \quad 1 \ 1 \ 1 \ 0 \ 0 \\ \hline \end{array}$$


Subtraction in 2's Complement System

Subtraction of 2's complement numbers is carried out in the same way as addition

- No need of separate hardware for addition and subtraction
 - get 2's complement (negate) of subtrahend
 - add it to minuend, result of this addition represent the difference

For example
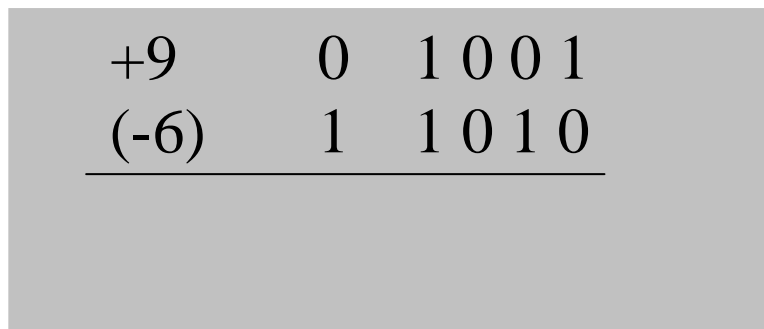
$$\begin{aligned} 9 - 6 &= 9 + (-6) \\ &= 9 + (2's \text{ complement of } 6) \\ &= \end{aligned}$$




A binary addition problem showing the sum of +9 and (-6) in 2's complement. The numbers are aligned by their least significant bits. A horizontal line is drawn under the second row. The result is not shown.

+9	0	1	0	0	1
(-6)	1	1	0	1	0
<hr/>					

Adder Circuits

Half adder performs addition of 2 bits.

Operand-1, X	Operand-2, Y	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

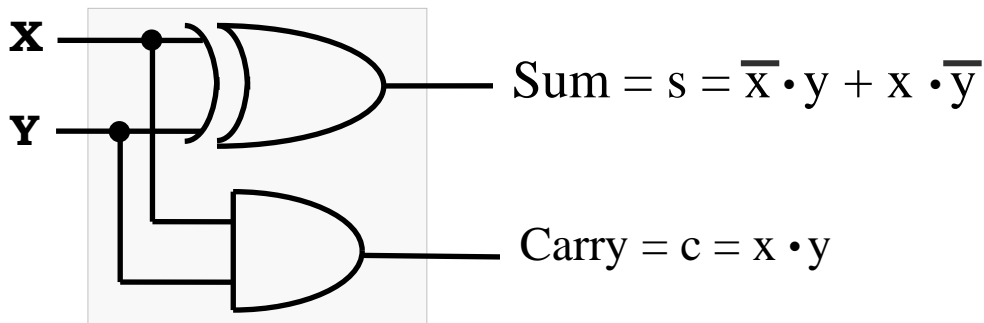


VHDL Code for Half Adder

```
library ieee ;
use ieee.std_logic_1164.all ;

entity half_adder is
    port ( x, y : in std_logic ;
          s, c : out std_logic ) ;
end half_adder ;

architecture dataflow_ha of half_adder is
begin
    s <= x xor y ;
    c <= x and y ;
end dataflow_ha;
```



1-Bit Full Adder

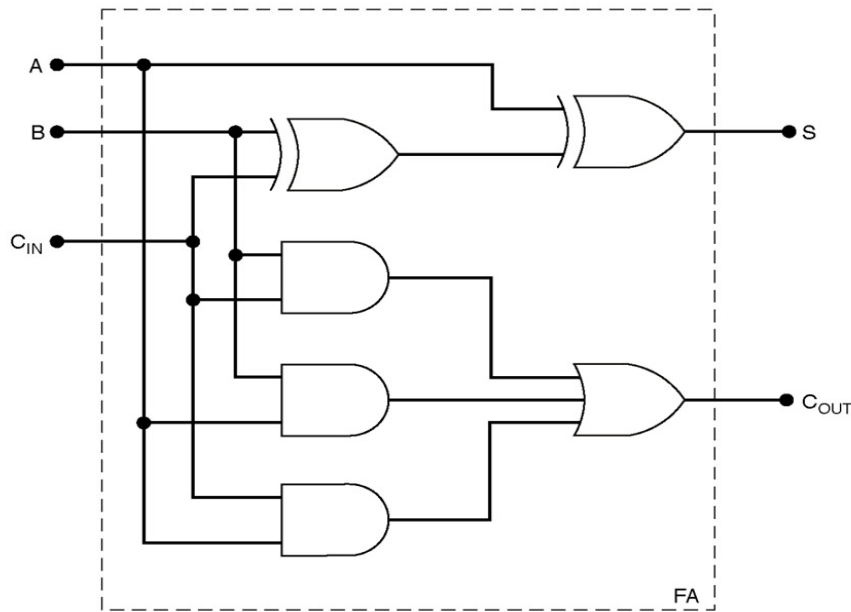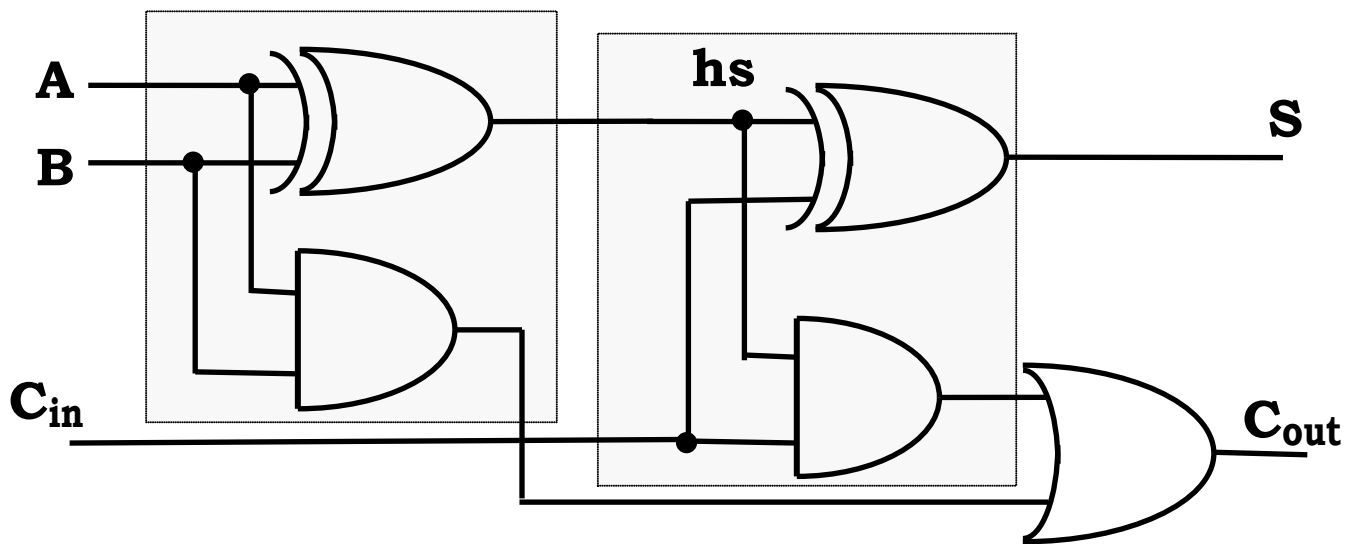

Two half adders and one OR gate can also implement a Full Adder.

$$S = (A \oplus B) \oplus C_{IN}$$

$$C_{OUT} = A.B + C_{IN}. (A \oplus B)$$



Full Adder

$$S = (A \oplus B) \oplus C_{IN}$$

$$C_{OUT} = A \cdot B + C_{IN} \cdot (A \oplus B)$$

VHDL Code of Full Adder

```
library ieee ;
use ieee.std_logic_1164.all ;




entity full_adder is
    port ( a, b, cin : in std_logic ;
          s, cout : out std_logic ) ;
end full_adder ;

architecture dataflow_fa of full_adder is

    component half_adder is
        port ( x, y : in std_logic ;
              s, c : out std_logic ) ;
    end component ;
    signal hs, hc, tc : std_logic

begin
    HA1: half_adder
        port map(a, b, hs, hc) ;
    HA2: half_adder
        port map(hs, cin, s, tc) ;
    cout <= tc or hc ;
end dataflow_fa ;
```

Multi-bit Adder

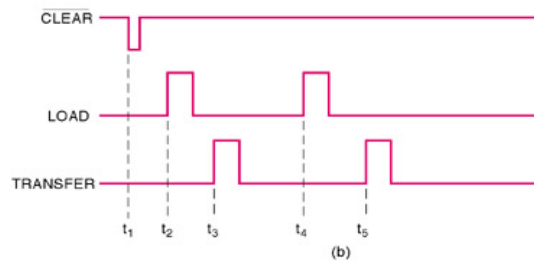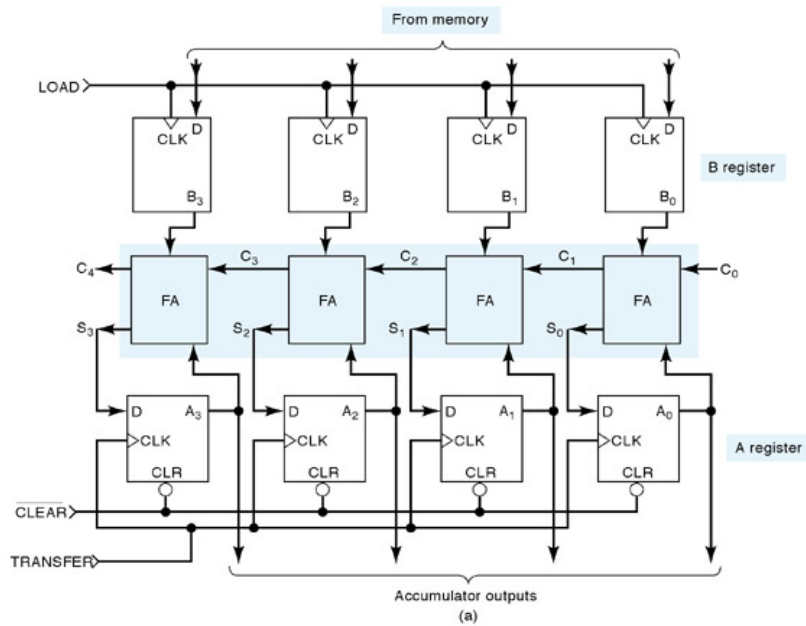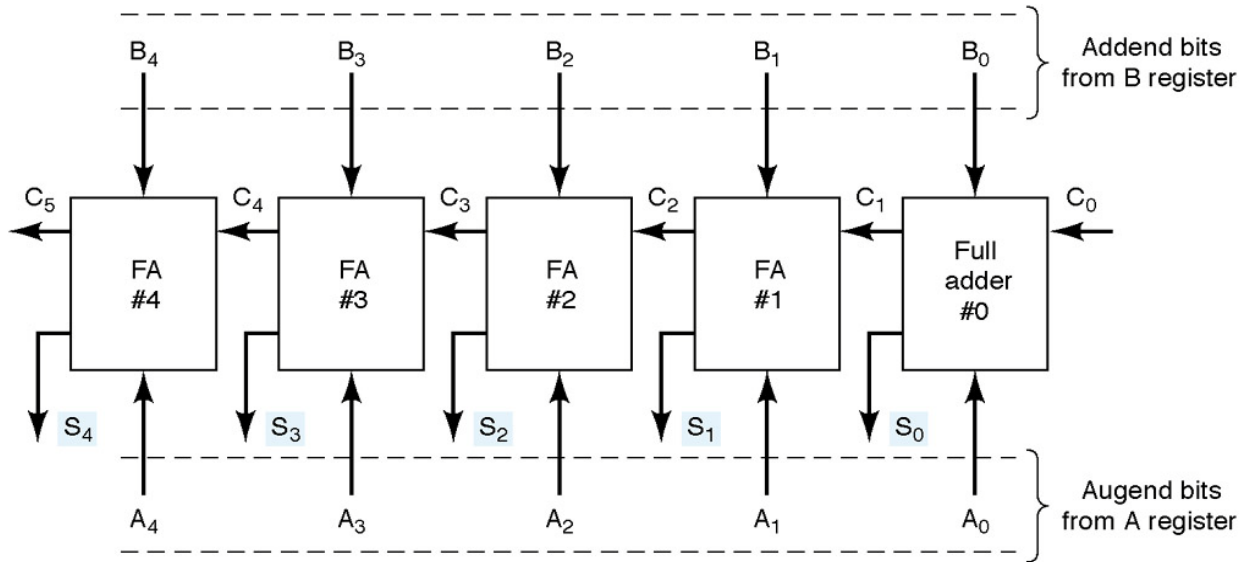

Speed limited by carry chain

4-bit Adder VHDL Code

```
library ieee ;
use ieee.std_logic_1164.all ;
entity adder_4 is
    port ( A, B : in std_logic_vector (3 downto 0) ;
          C0 : in std_logic ;
          S : out std_logic_vector (3 downto 0) ;
          C4 : out std_logic ) ;
end adder_4 ;
architecture dataflow_add4 of adder_4 is
    component full_adder is
        port ( a, b, cin : in std_logic ;
              s, cout : out std_logic ) ;
    end component ;
    signal C : std_logic_vector (4 downto 0) ;
begin
    C(0) <= C0
    BIT0: full_adder
        port map(B(0), A(0), C(0), S(0), C(1)) ;
    BIT1: full_adder
        port map(B(1), A(1), C(1), S(1), C(2)) ;
    BIT2: full_adder
        port map(B(2), A(2), C(2), S(2), C(3)) ;
    BIT3: full_adder
        port map(B(3), A(3), C(3), S(3), C(4)) ;
    C4 <= C(4) ;
end dataflow_add4 ;
```

Ripple Addition

Typical Ripple Carry Addition is a Serial Process:

- Addition starts by adding LSBs of the augend and addend.
- Then next position bits of augend and addend are added along with the carry (if any) from the preceding bit.
- This process is repeated until the addition of MSBs is completed.

Carry Propagation

- Speed of a ripple adder is limited due to carry propagation or carry ripple.
- Sum of MSB depends on the carry generated by LSB.

Carry Lookahead Adder

Faster Adders Limit the Carry Chain


- 2-level AND-OR logic.
 2^n product terms
- 3 or 4 levels of logic, carry look-ahead

A Carry look-ahead adder avoids carry propagation delay by using additional logic circuit.

Looks at the lower order bits of operands and determine if a higher-order carry is to be generated

$$\begin{aligned} \text{The Sum bit } S_i &= A_i \oplus B_i \oplus C_i \\ C_{i+1} &= g_i + p_i C_i \end{aligned}$$

Carry Lookahead Adder

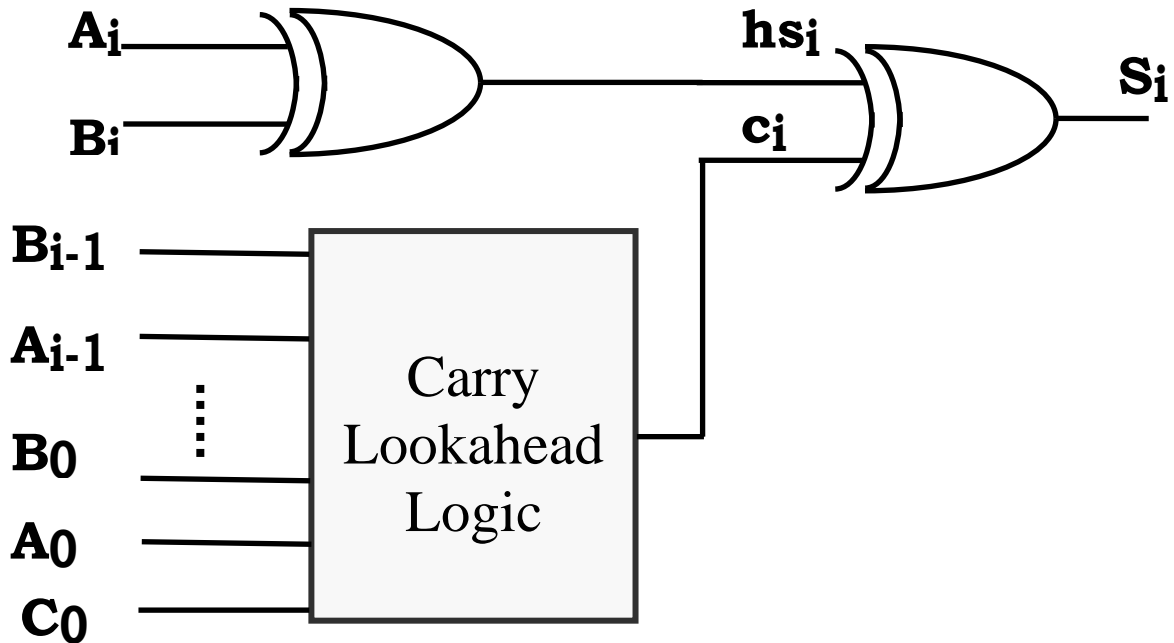

$$C_1 = g_0 + p_0 C_0$$


$$C_2 = g_1 + p_1 C_1 = g_1 + p_1 g_0 + p_1 p_0 C_0$$


$$C_3 = g_2 + p_2 C_2 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 C_0$$

$$C_4 = C_{OUT} = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 C_0$$


4-bit Carry Look-ahead Adder

74x283

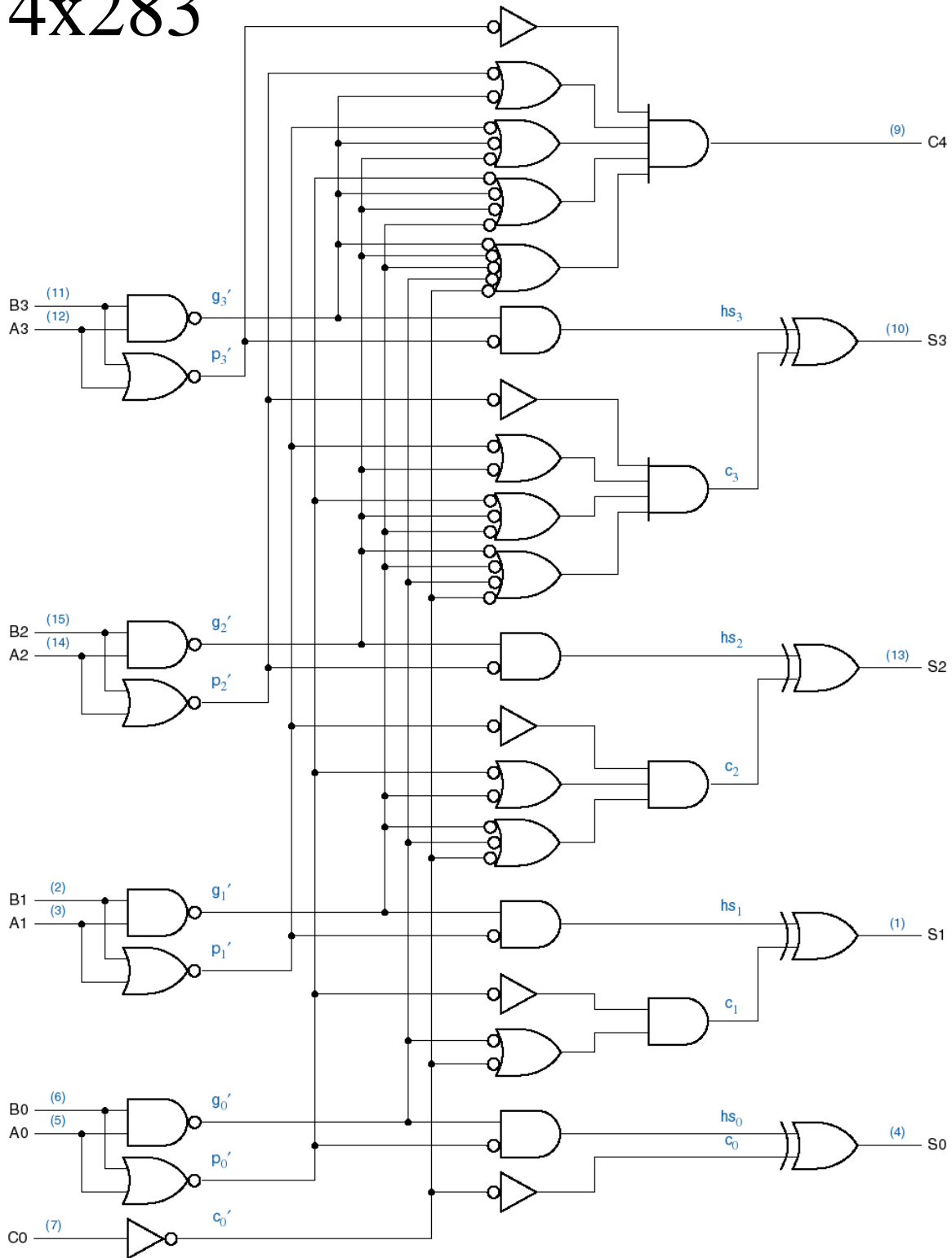

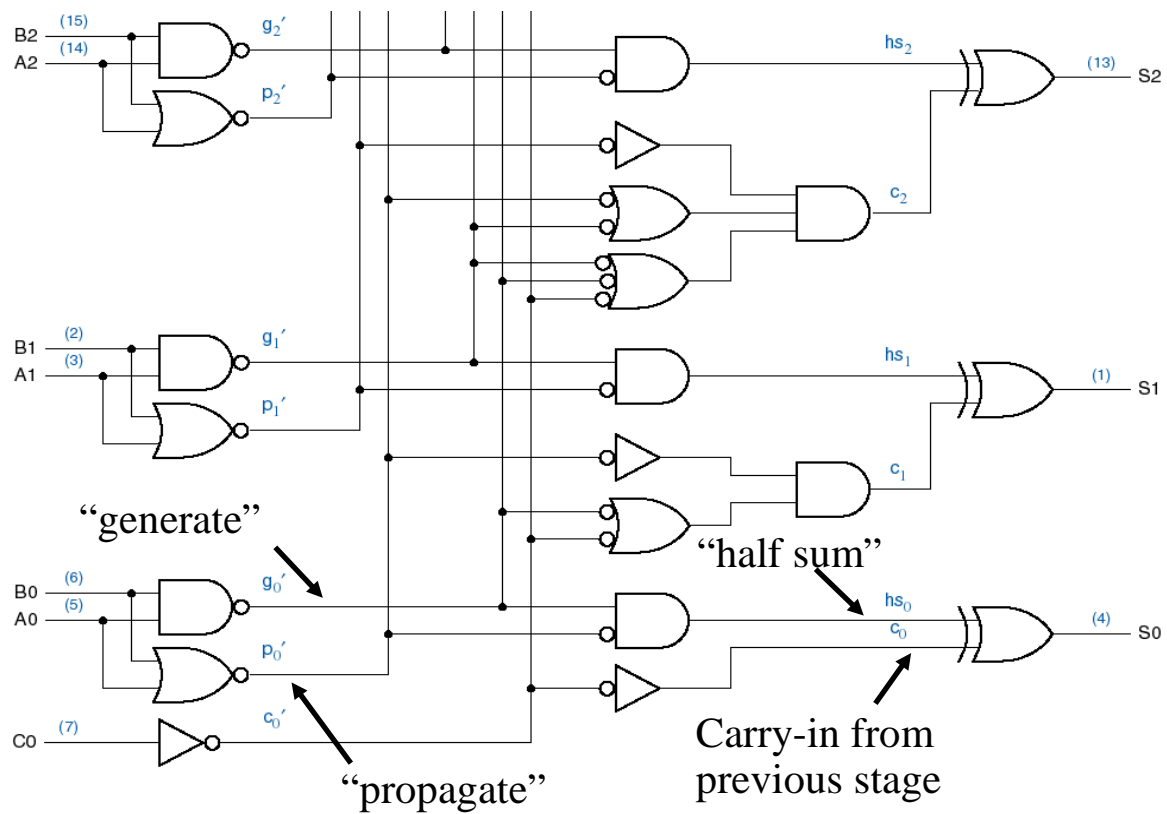

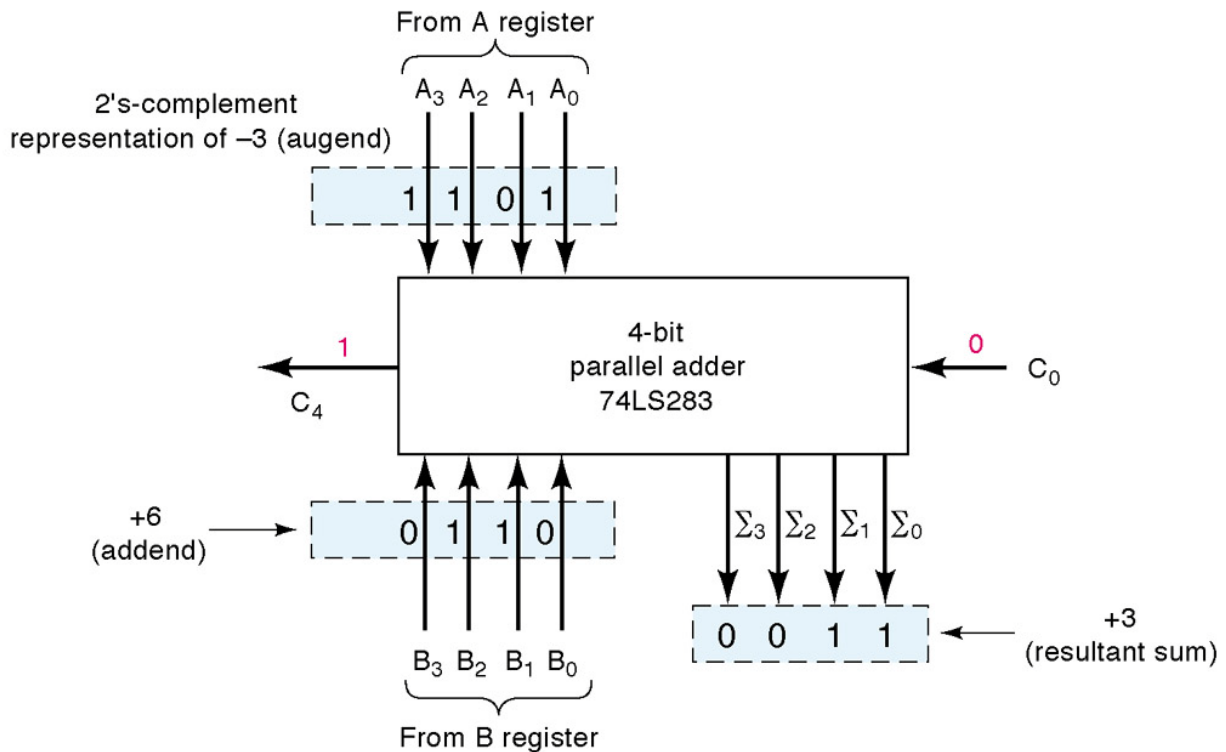Addition of +ve/-ve numbers in 2's-complement



Subtraction

Negative numbers can be added by first converting them to 2's complement form.


Subtraction is the same as addition of the two's complement numbers.

- The two's complement is a bit-by-bit complement plus 1.
- Therefore: $X - Y = X + Y' + 1$

If the result is negative then get 2's complement of the result.

Adder circuit can be modified to perform both addition and subtraction in a 2's complement system

2's Complement Addition and Subtraction

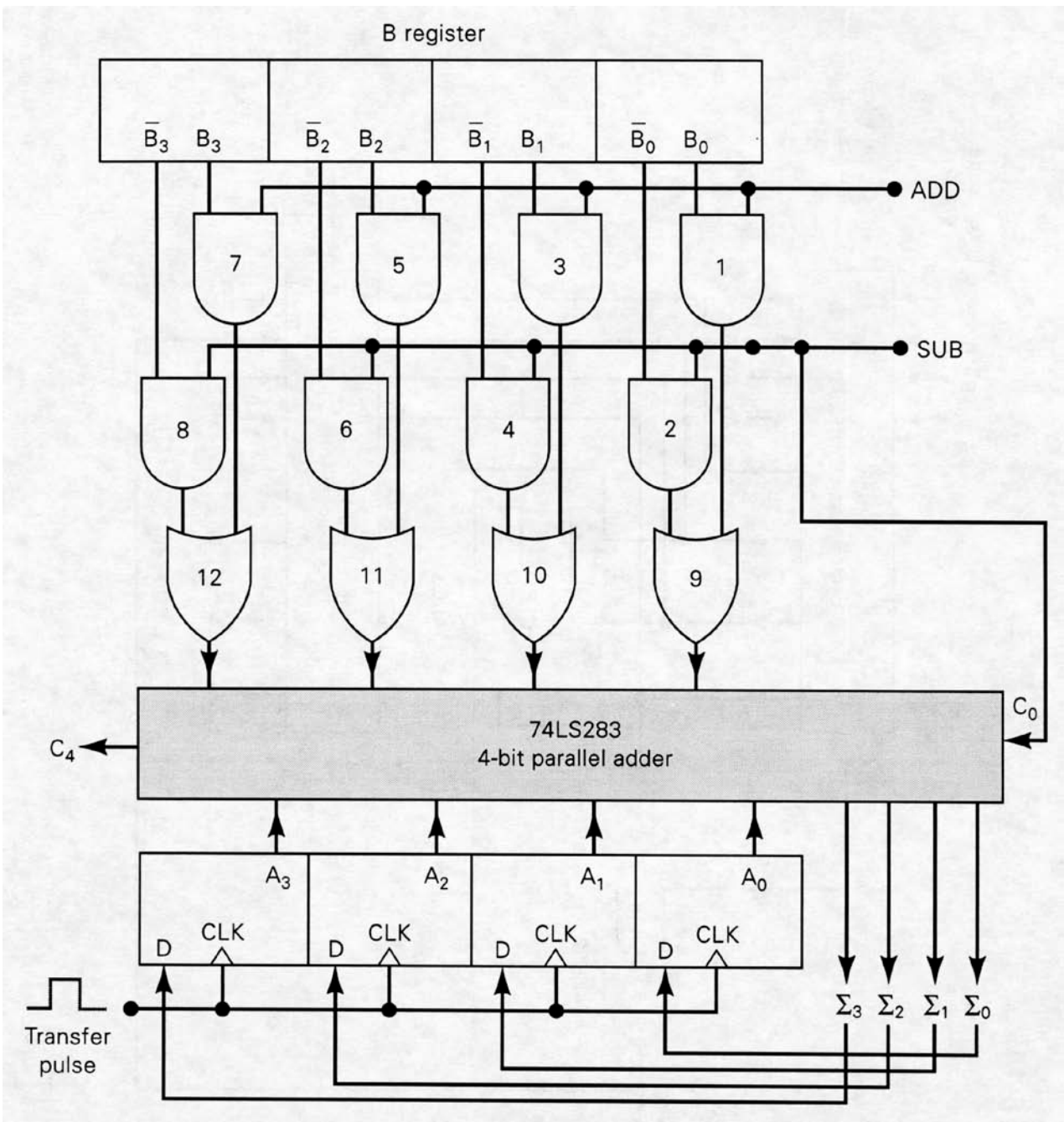

Adder-Subtractor


2's Complement System Addition

Straight forward


2's Complement System Subtraction

- Minuend and Subtrahend are in registers A and B respectively
- SUB = 1 enables AND gates 2, 4, 6, 8
- ADD = 0 disables AND gates 1, 3, 5, 7
- It connects the complement of subtrahend to port B of LS283
- $C_0 = 1$ produces 2's complement of subtrahend during addition
- Transfer pulse adds minuend and 2's complement of subtrahend (i.e. equivalent to subtraction)


ALU Architecture

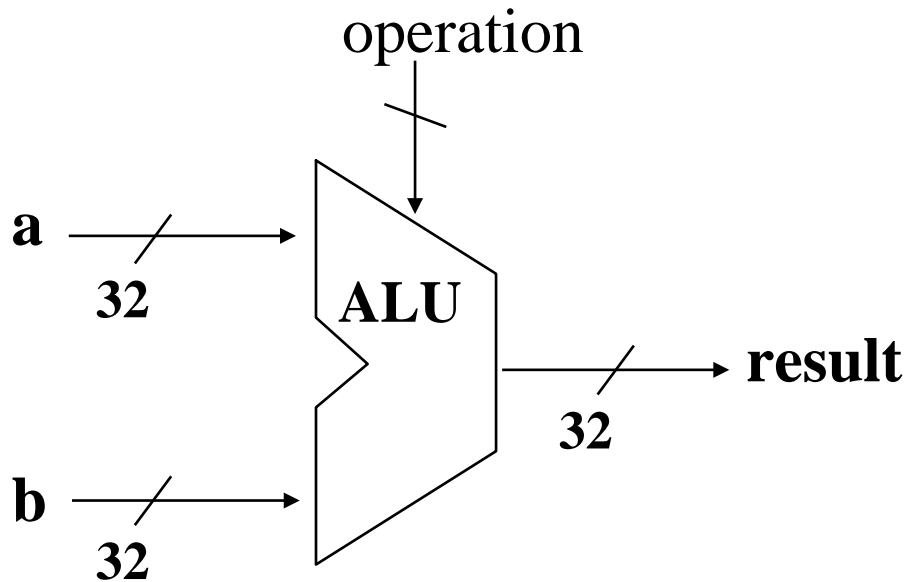

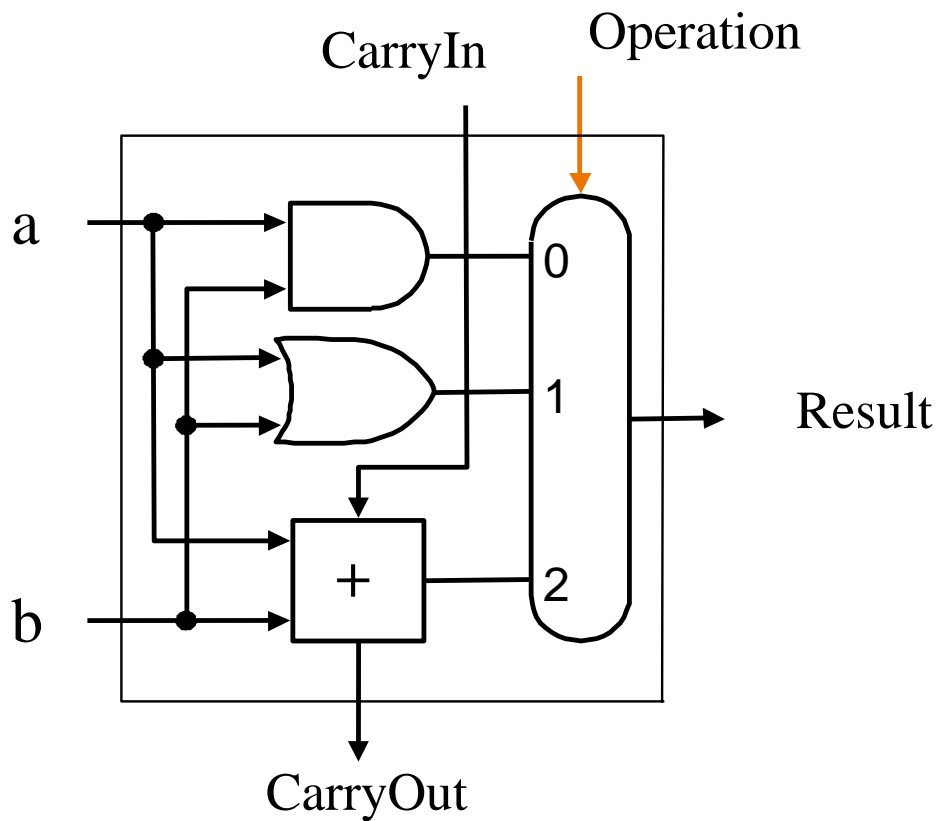1-bit ALU that performs AND, OR and Addition




32-bit ALU

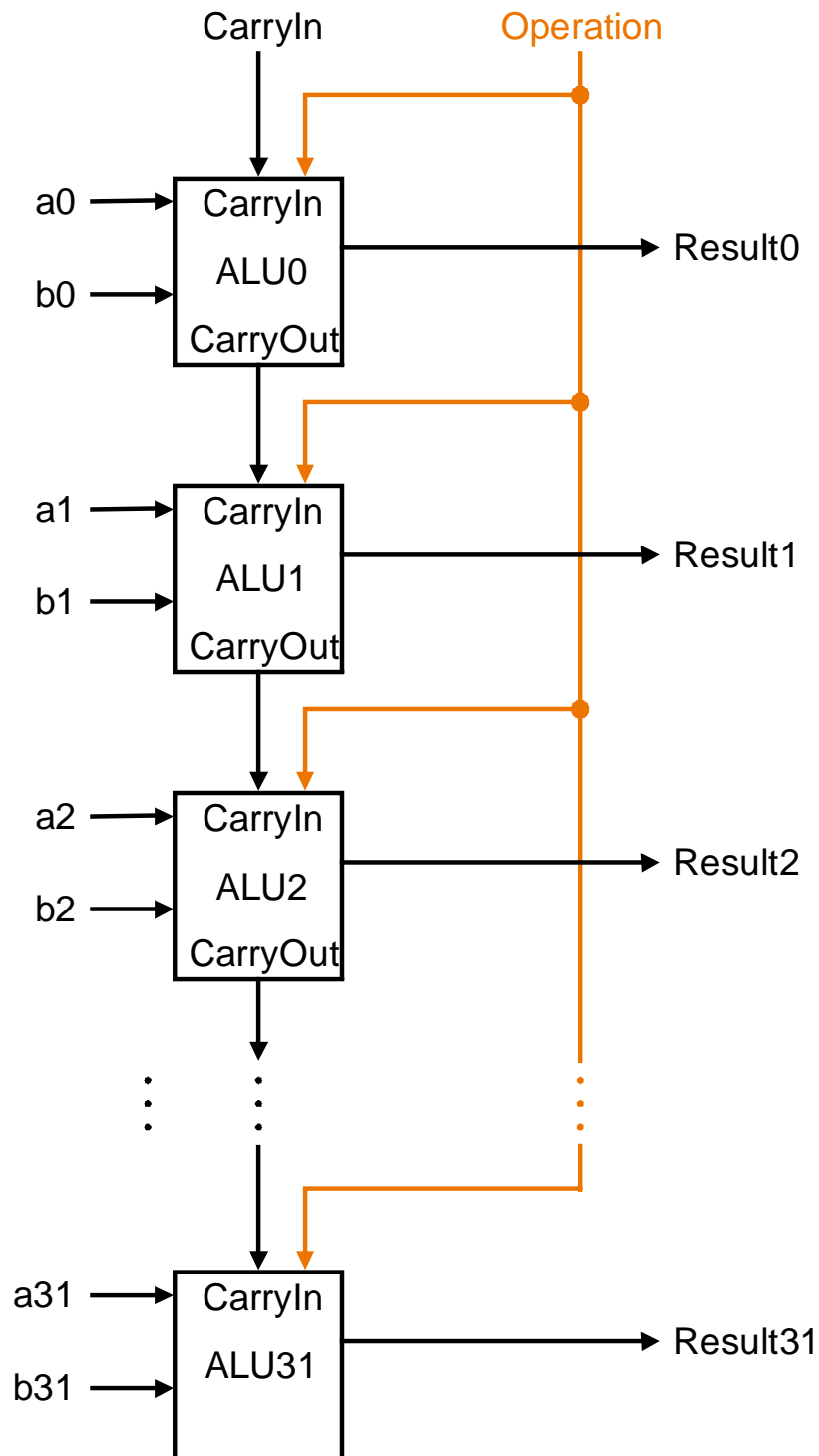

ALU for MIPS-Processor

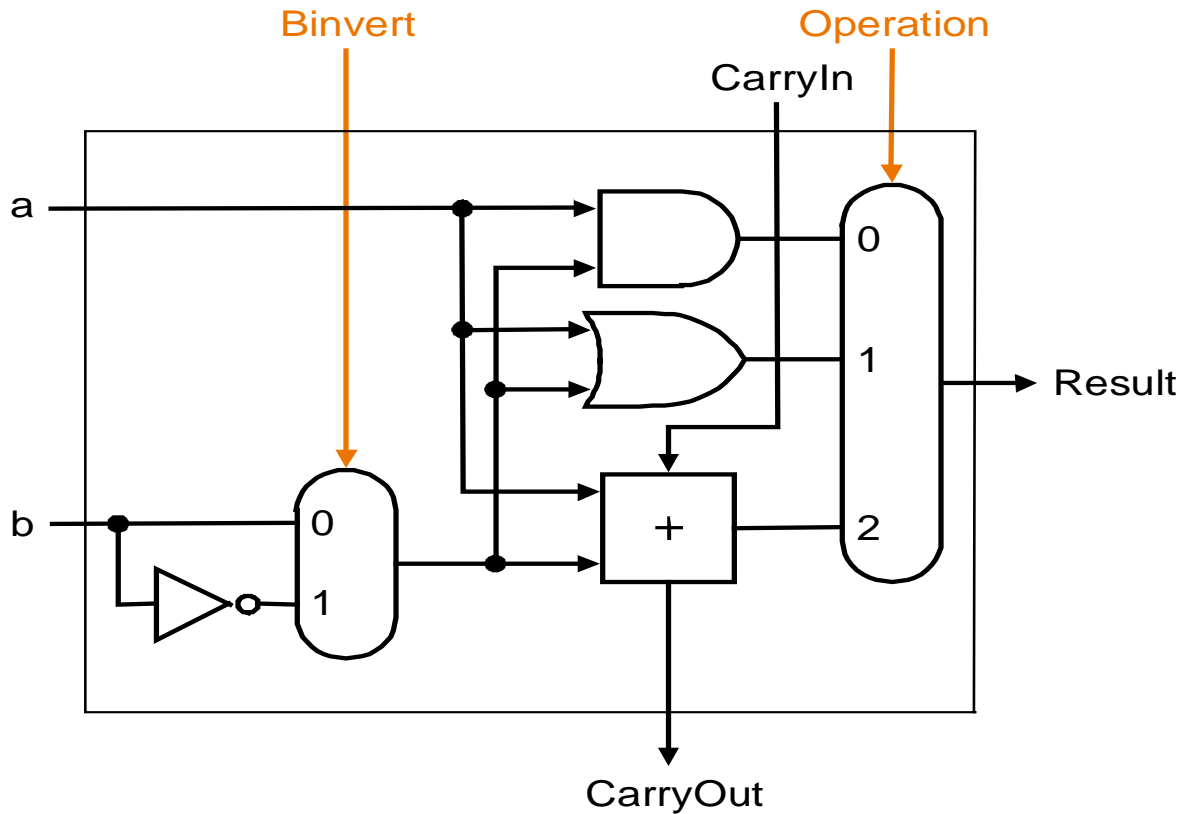Subtraction Option: $a - b = a + \bar{b} + 1$



Support the set-on less-than instruction (**slt**)


– **slt** is an arithmetic instruction.

slt \$t5, \$t6, \$t7

Need to test for equality (**beq** \$t6, \$t7, Label)


Use subtraction: $(a - b) = 0$ implies $a = b$

Supporting the `slt` Instruction

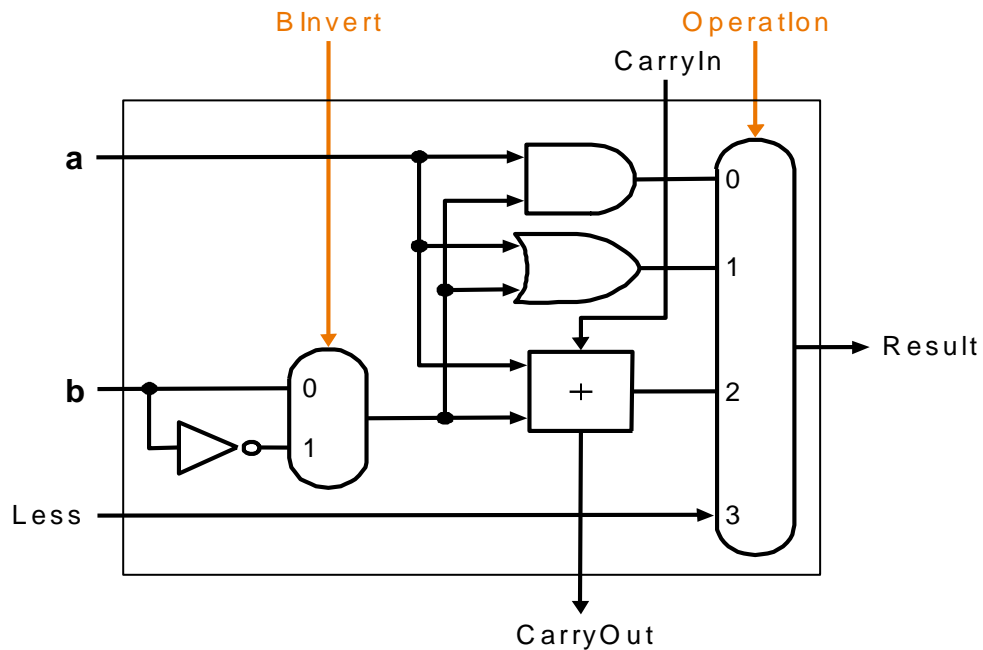

Overflow Detection

Set Overflow output to 1 when $a < b$

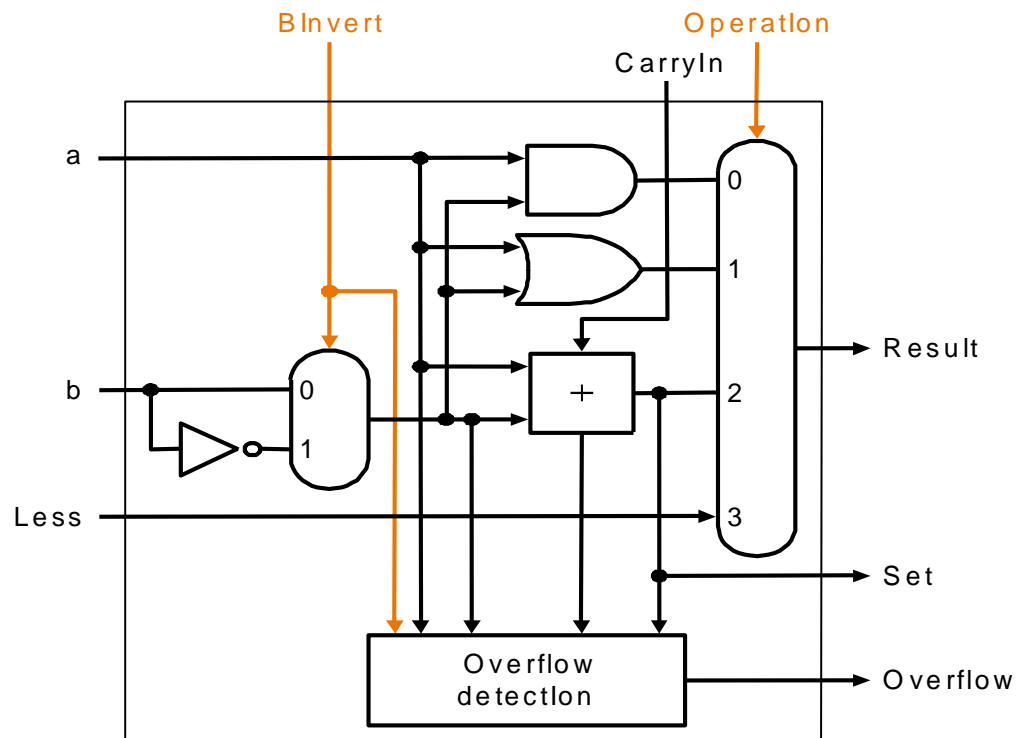

Detecting Overflow

No Overflow

- ◆ By adding a positive (+ve) and a negative (-ve) number.
- ◆ subtracting numbers of the same signs.

Overflow occurs when value affects the sign.

- ◆ By adding two positives yields a negative result.
- ◆ Adding two negatives gives a positive.
- ◆ Subtract a -ve from a +ve and get a negative.
- ◆ Subtract a +ve from a -ve and get a positive.

Consider the operations $A + B$ and $A - B$

- ◆ Can overflow occur if B is 0 ?
- ◆ Can overflow occur if A is 0 ?

Effects of Overflow


- An exception (interrupt) occurs.
 - ◆ Control jumps to predefined address for exception.
 - ◆ Interrupted address is saved for resumption.

If there is no need to detect overflow


- new MIPS-CPU instructions: `addu`, `addiu`, `subu`

32-bit ALU

Overflow and `slt` Supported

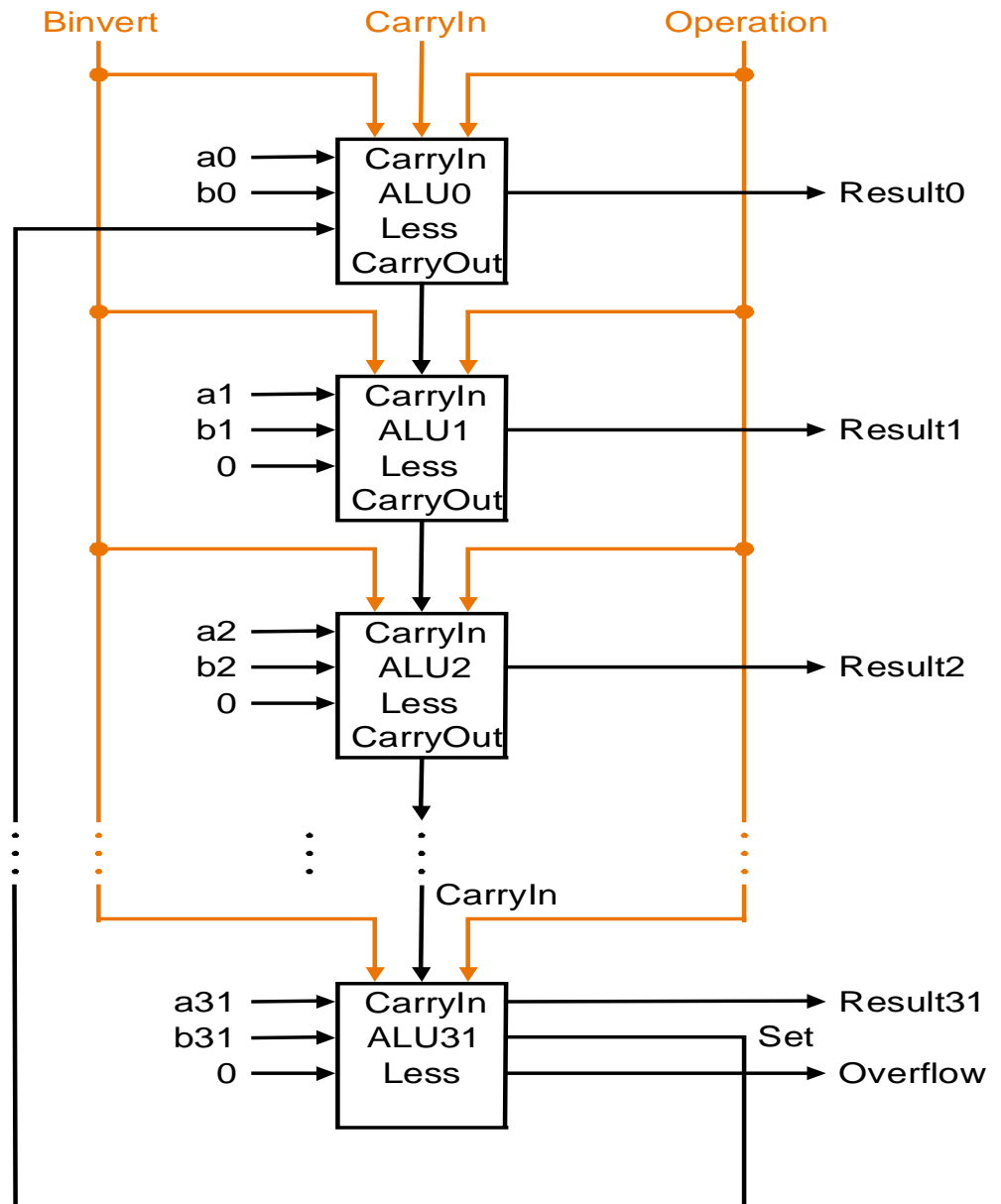

Test for Equality

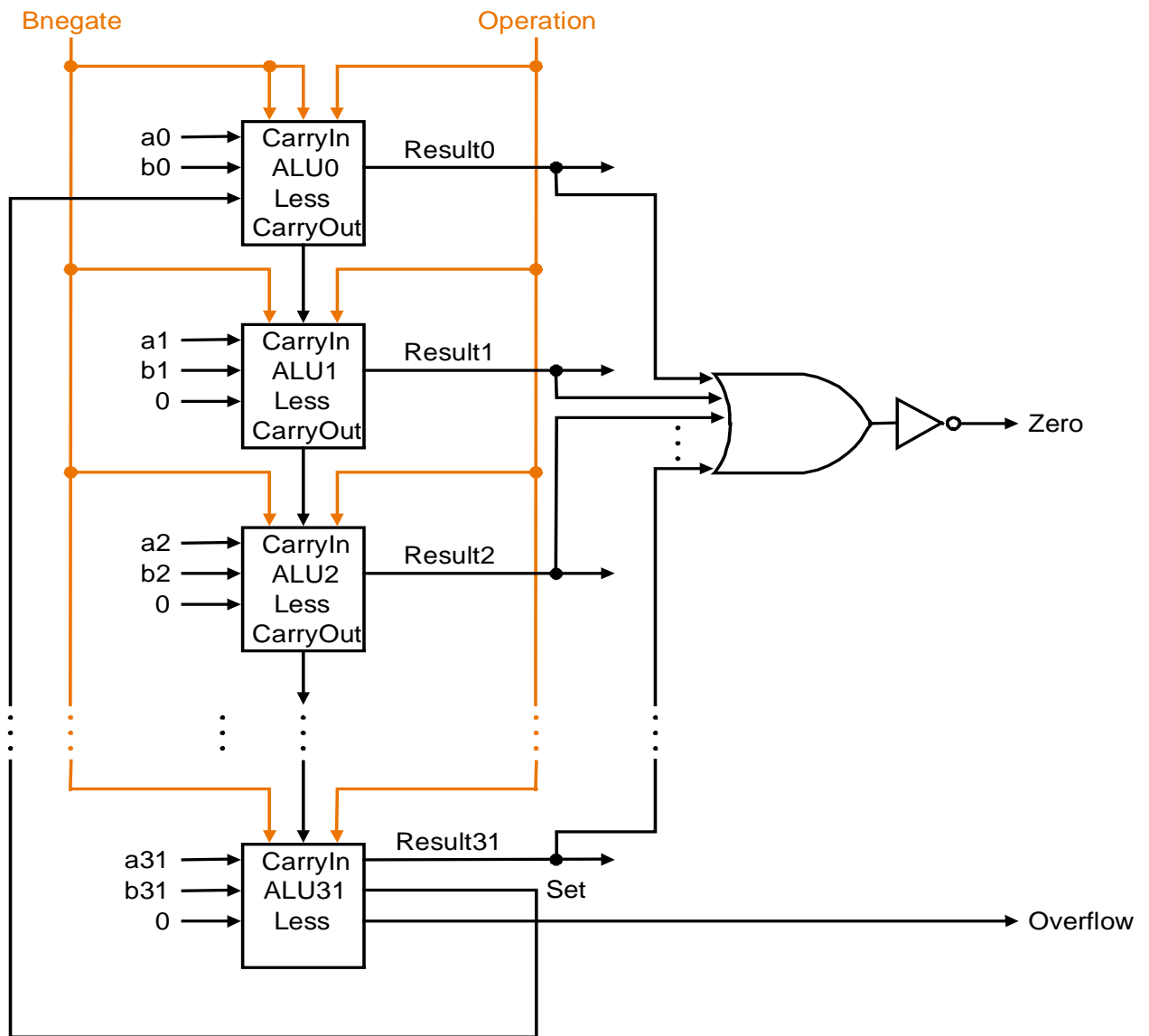

Notice the control lines

000 = and

001 = or

010 = add

110 = subtract

111 = slt

Multiplication

Binary Multiplier

Product of two 4-bit numbers is an 8-bit number

multiplicand	1101 (13)
multiplier	* 1011 (11)

10001111 (143)


4-bit Multiplication

			A3	A2	A1	A0	
			B3	B2	B1	B0	
			A3B0	A2B0	A1B0	A0B0	
		A3B1	A2B1	A1B1	A0B1		
	A3B2	A2B2	A1B2	A0B2			
A3B3	A2B3	A1B3	A0B3				
S7	S6	S5	S4	S3	S2	S1	S0


4-Bit Multiplier Circuit

Unsigned Combinational Multiplier

4 x 4 Array of Building Blocks (Cells)

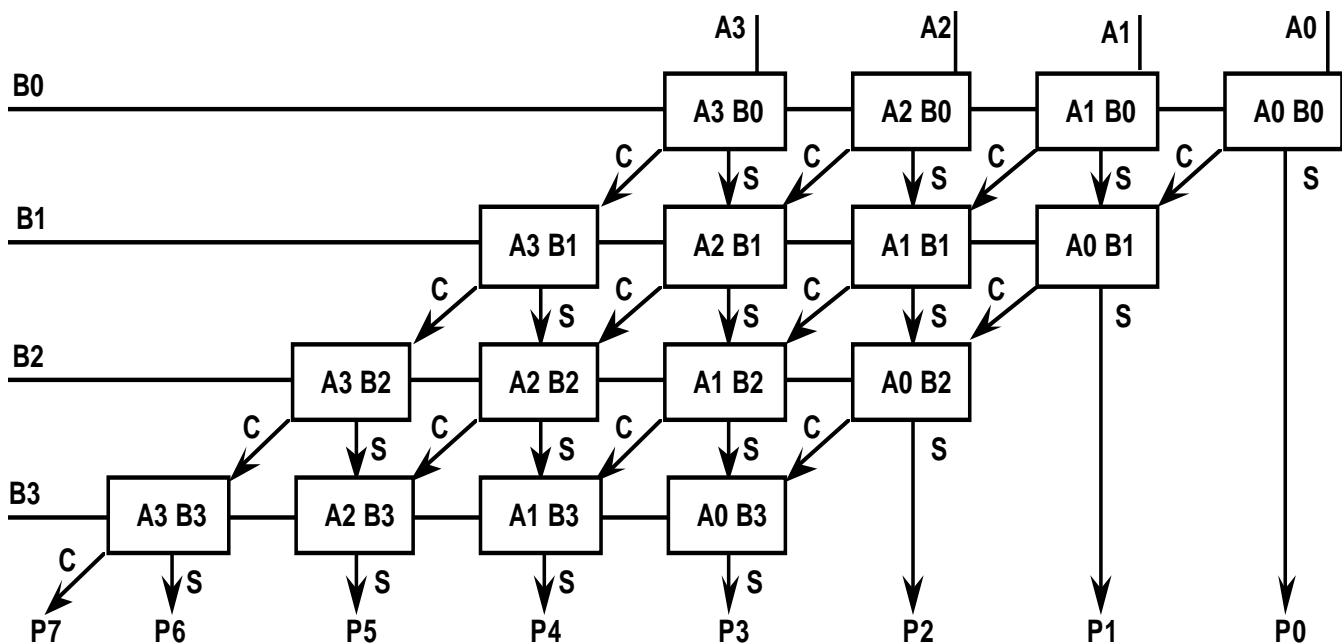


Building Block/Cell

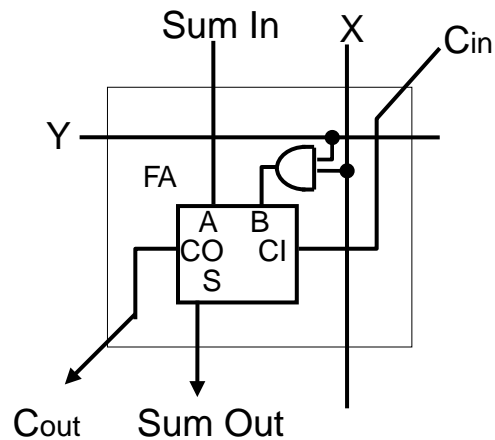

Unsigned Shift-Add Multiplier


(version 1)

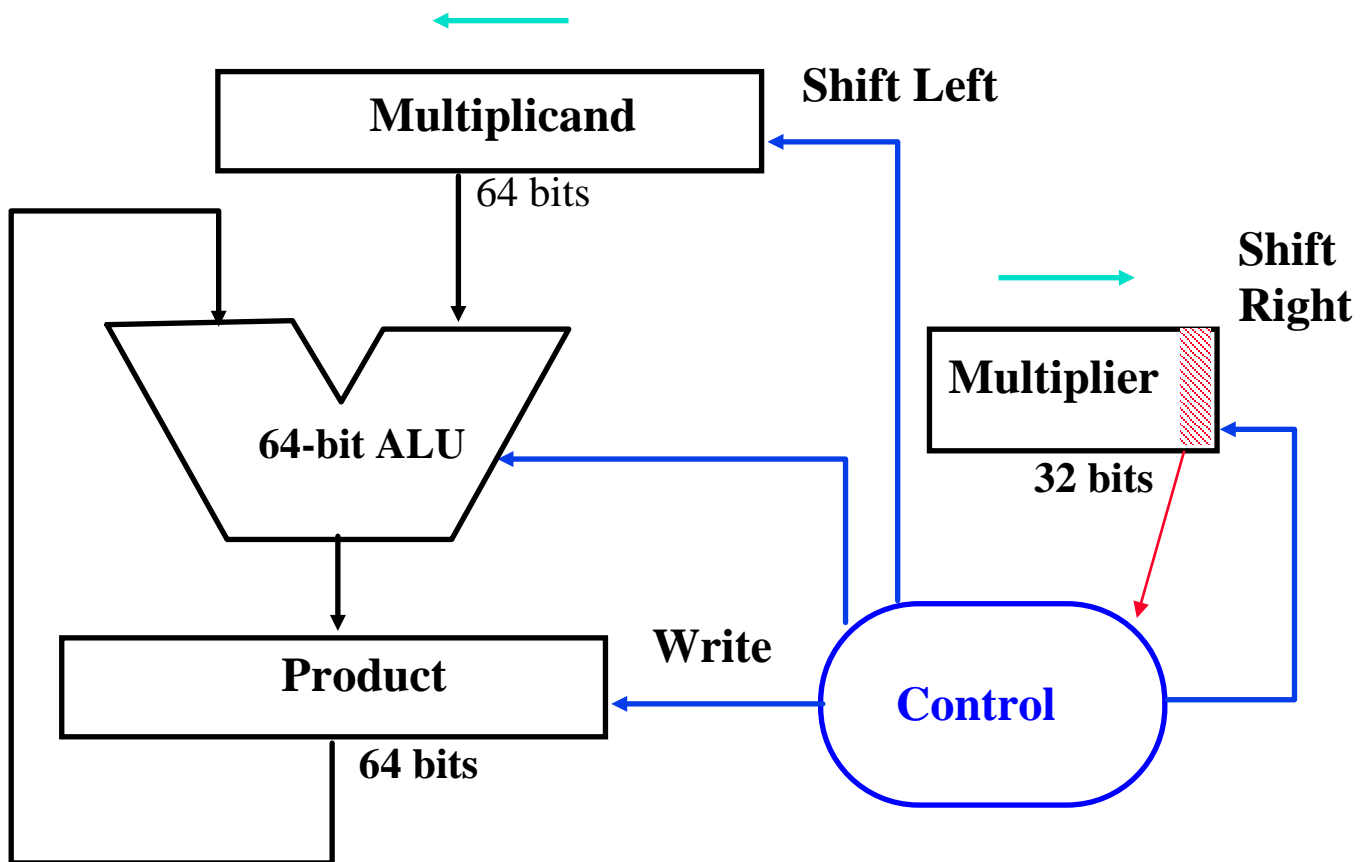

Multiplier = datapath + control

Unsigned Shift-Add Multiplier

(version 1)

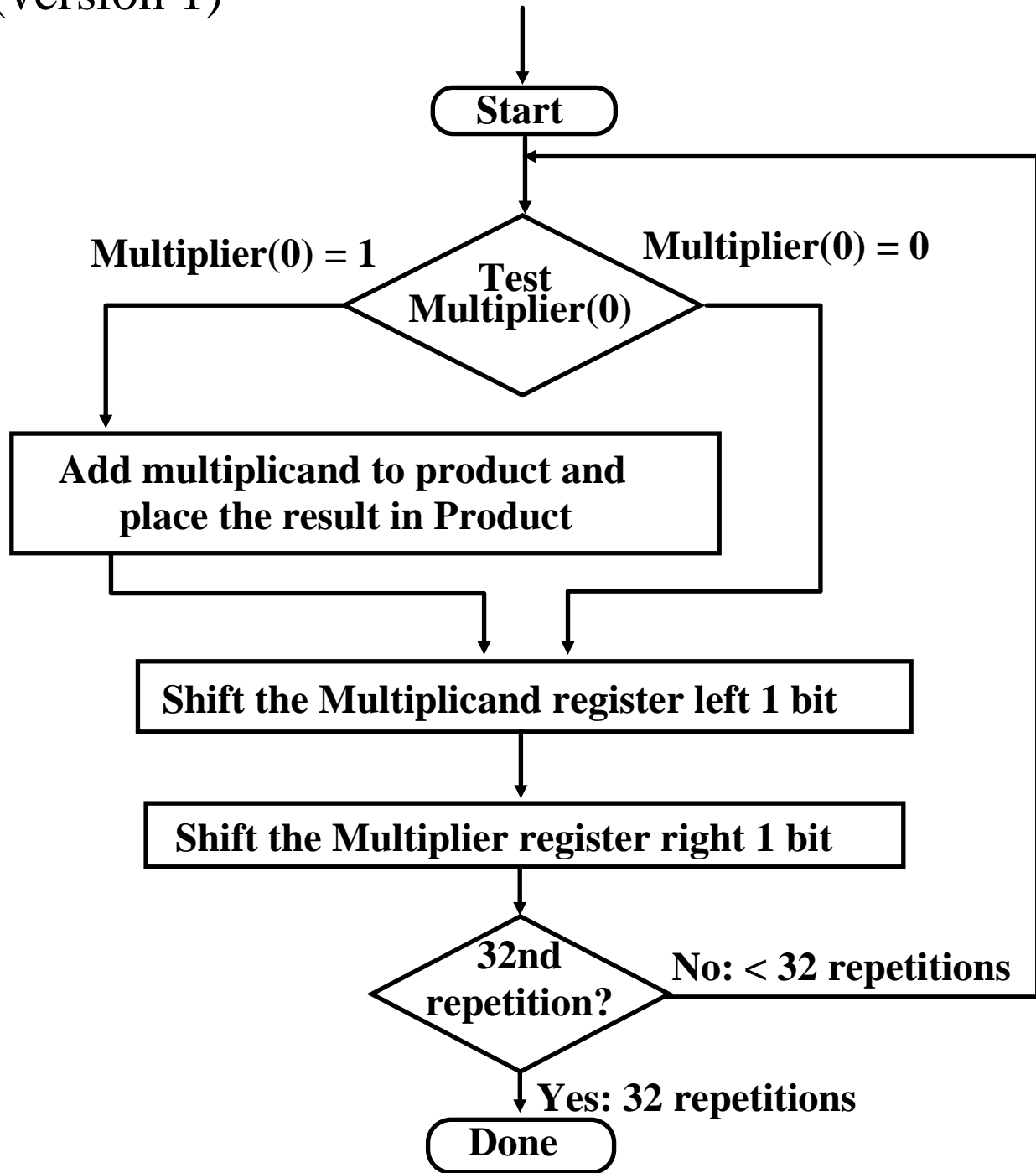

Unsigned Shift-Add Multiplier

Product	Multiplier	Multiplicand
0000 0000	0011	0000 0010

1 clock per cycle => 100 clocks/multiply.

Ratio of multiply to add 5:1 to 100:1

1/2 bits in multiplicand always 0.

=> 64-bit adder is wasted.

0 bits are inserted in left of the multiplicand as shifted.

=> least significant bits of product never changed once formed

Multiplier


(version 2)

32-bit Multiplicand register

32-bit ALU

64-bit Product register


32-bit Multiplier register

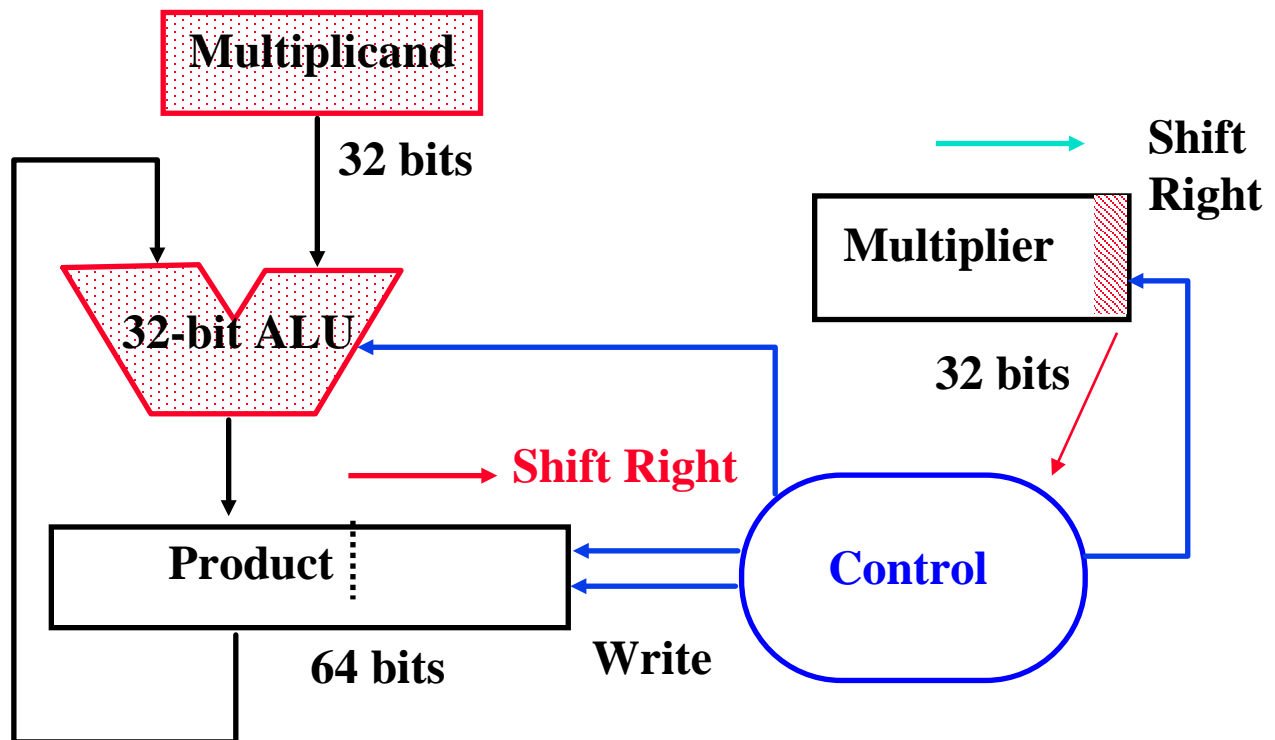

Multiplier Algorithm


(version 2)

Multiplier	Multiplicand	Product
0011	0010	0000 0000

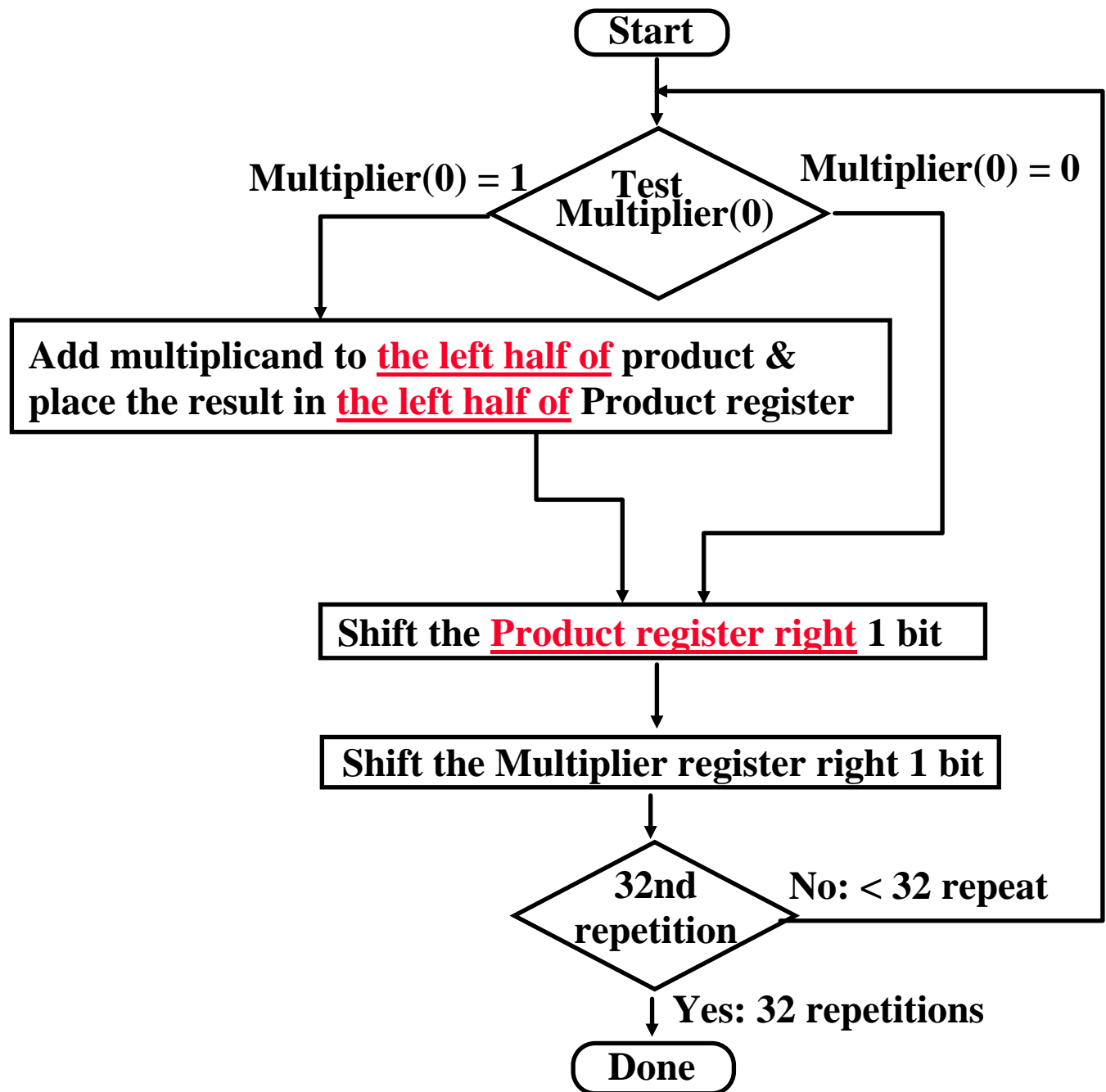

Multiplication Process

<u>Product</u>	<u>Multiplier</u>	<u>Multiplicand</u>
0000 0000	0011	0010

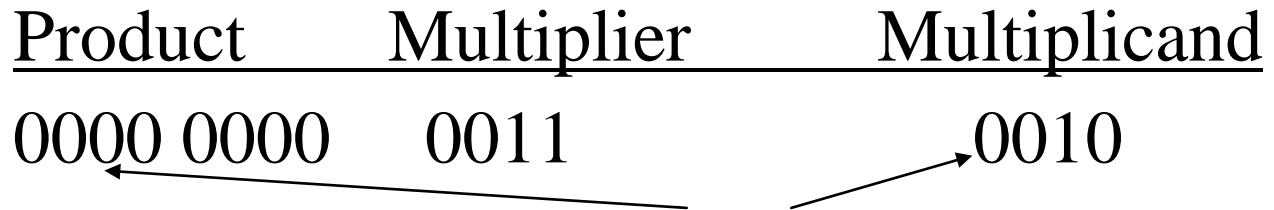

Product register wastes space that exactly matches with the size of multiplier

=> combine Multiplier register and Product register.

Integer Multiplication in MIPS

In MIPS, we multiply registers:

32-bit value x 32-bit value = 64-bit value

Syntax of Multiplication (signed):

mult *register1, register2*

- Multiplies 32-bit values in those registers & puts 64-bit product in special registers hi & lo (separate from the 32 general purpose registers)
- Use mfhi move from hi and move from mflo.

Example in C: $a = b * c$; Let b be \$s2; let c be \$s3; and let a be \$s0 and \$s1 (since it may be up to 64 bits)

```
mult $s2, $s3    # b*c
mfhi $s0         # upper half of product into $s0
mflo $s1         # lower half of
                 # product into $s1
```

Integer Division

$$\begin{array}{r}
 \text{Divisor } 1000 \overline{) 1001010} \\
 \underline{-1000} \\
 10 \\
 101 \\
 1010 \\
 \underline{-1000} \\
 10 \text{ Remainder} \\
 \text{(or Modulo result) Dividend}
 \end{array}$$

= Quotient x Divisor + Remainder

MIPS Division

div *register1, register2*

Divides 32-bit register-1 by 32-bit register-2 and puts remainder of division in **hi**, quotient in **lo**
 Implements C division (/) and modulo (%)


Example in C: $a = c / d; b = c \% d;$ In MIPS:

$a \ll \$s0; b \ll \$s1; c \ll \$s2; d \ll \$s3$ `div $s2,$s3` # $lo = c/d,$
 $hi = c \% d$

`mflo $s0` # *get quotient*

`mfhi $s1` # *get remainder*

Division

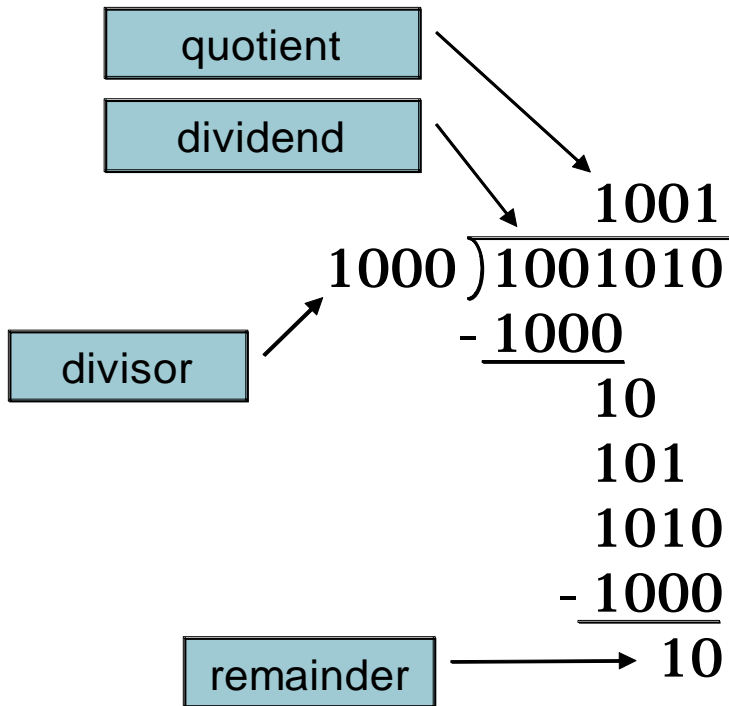


n-bit operands yield *n*-bit quotient and remainder

Check for 0 divisor
 Long division approach
 If divisor \leq dividend bits
 * 1 bit in quotient, subtract
 * Otherwise 0 bit in quotient, bring down next dividend bit
 Restoring division
 * Subtract, and if remainder is < 0 , then add divisor back


Signed division

- * Divide using absolute values
- * Adjust sign of quotient and remainder as required


Divisor Hardware

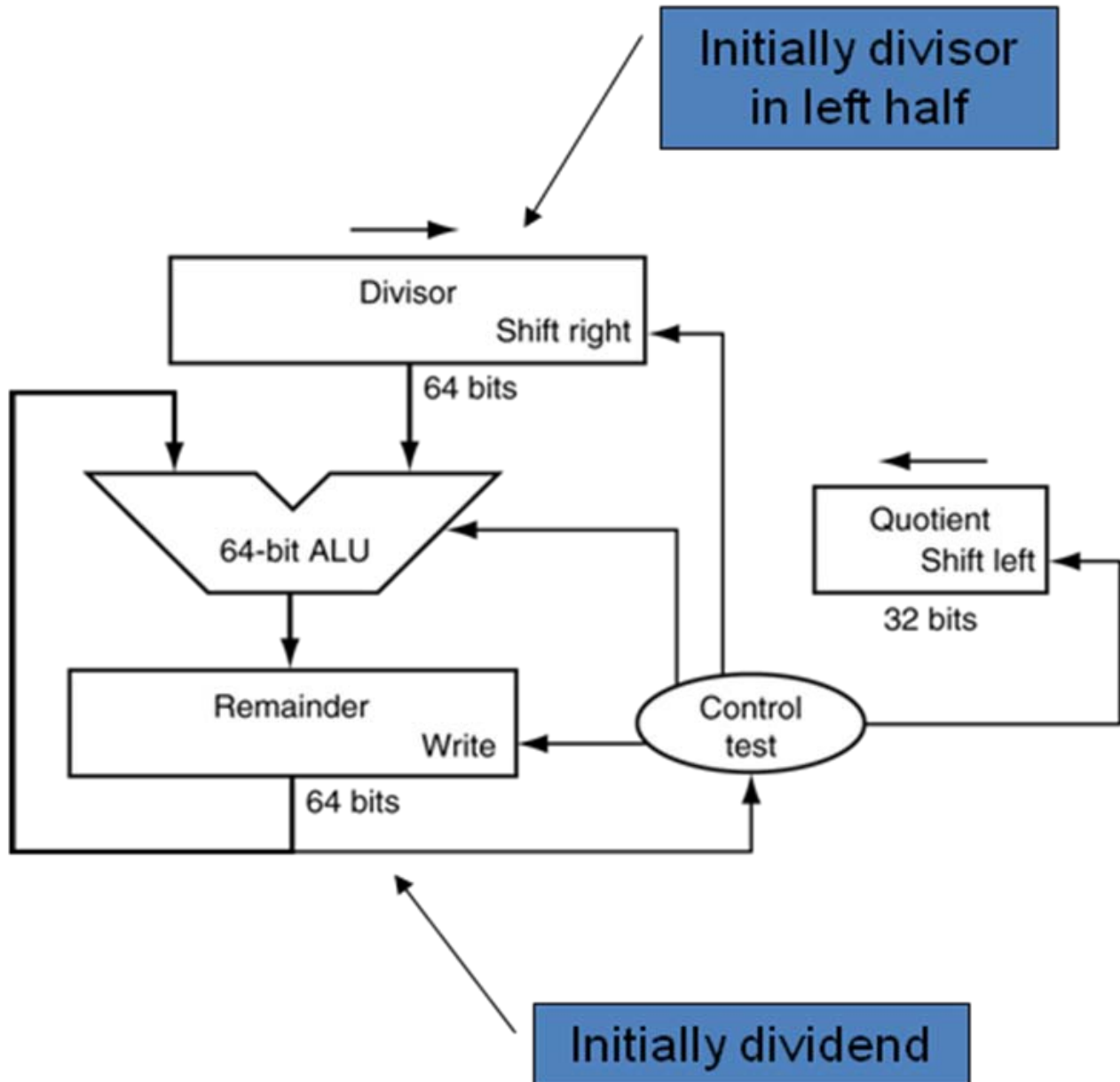

Division Algorithm

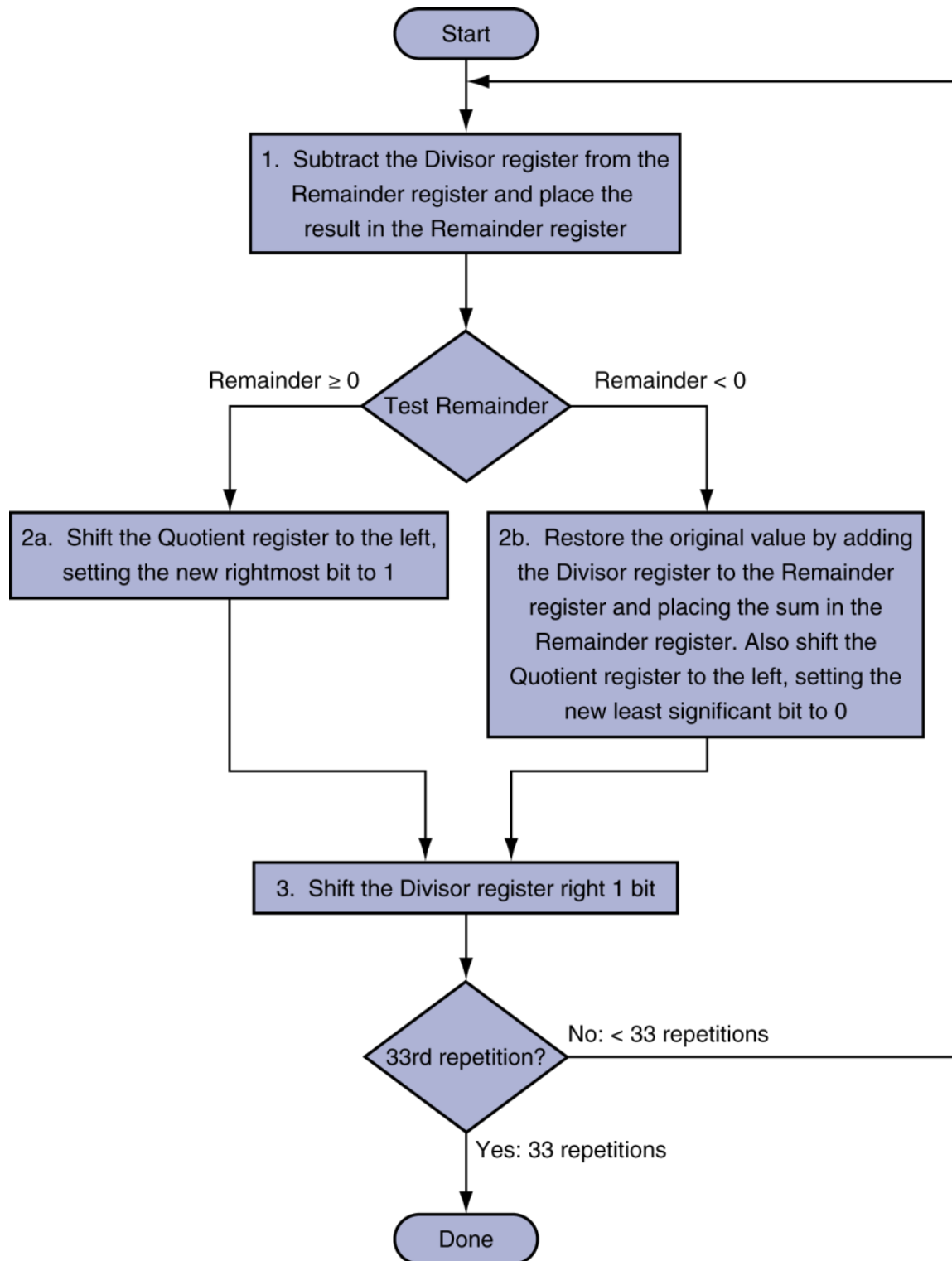

Optimal Division Hardware

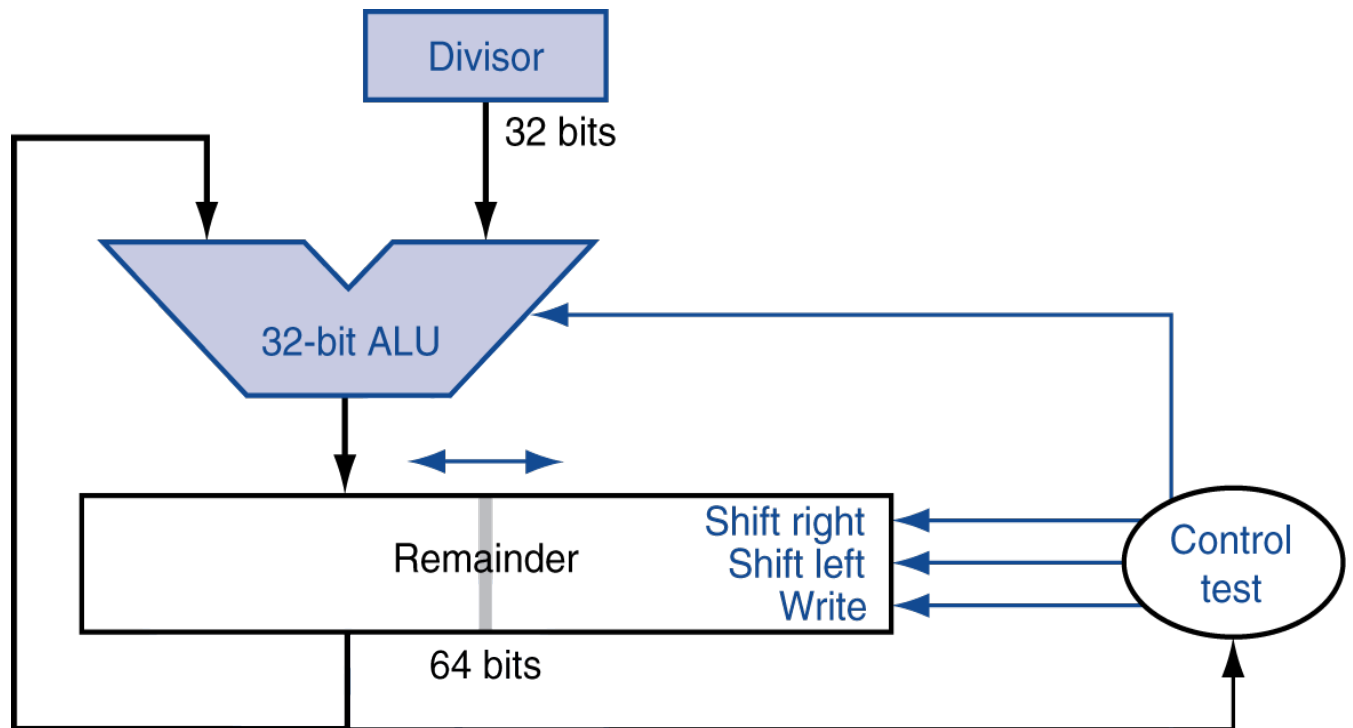


One cycle per partial-remainder subtraction

Looks a lot like a multiplier!

Same hardware can be used for both multiplication and division.

Floating Point Arithmetic

Scientific Notation (in Decimal)

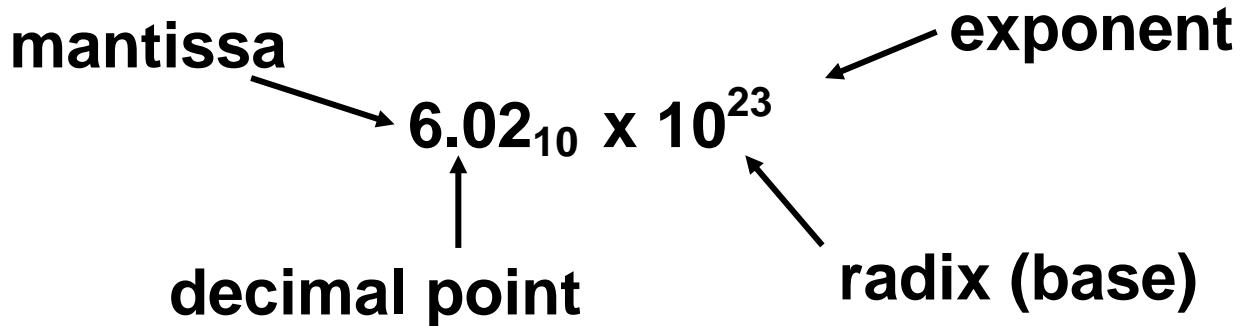


Normalized form: no leading 0s

(exactly one digit to left of decimal point)

Alternatives to representing 1/1,000,000,000

Normalized: 1.0×10^{-9}

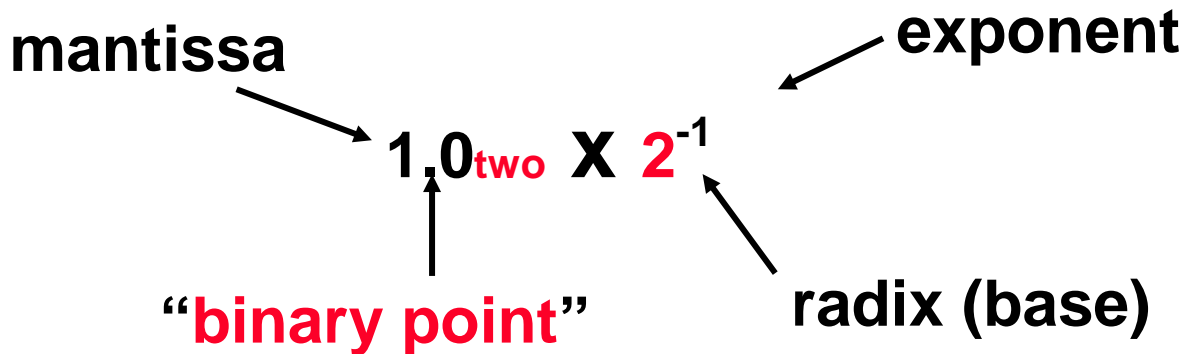Not normalized: 0.1×10^{-8} , 10.0×10^{-10}



Computer arithmetic that supports it called floating point, because it represents numbers where binary point is not fixed, as it is for integers


- Declare such variable in C as float

Floating Point Arithmetic

- Floating Point numbers approximate values that we want to use.
- IEEE 754 Floating Point Standard is most widely accepted attempt to standardize interpretation of such numbers
- Every desktop or server computer sold since ~1997 follows these conventions

Single Precision Floating Point

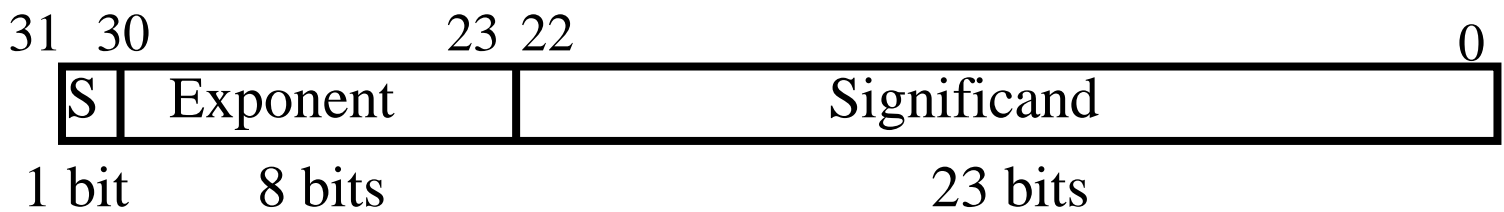Normal Format: $+1.xxxxxxxxxx_{two} $\times 2^{yyy}$ _{two}$




$$(-1)^S \times (1 + \text{Significand}) \times 2^{(\text{Exponent}-127)}$$

S represents **Sign**, **Exponent** represents **y**'s
Significand represents **x**'s

Represent numbers as small as 2.0×10^{-38}
to as large as 2.0×10^{38}

Double Precision Floating Point Representation

Next Multiple of Word Size (64 bits)

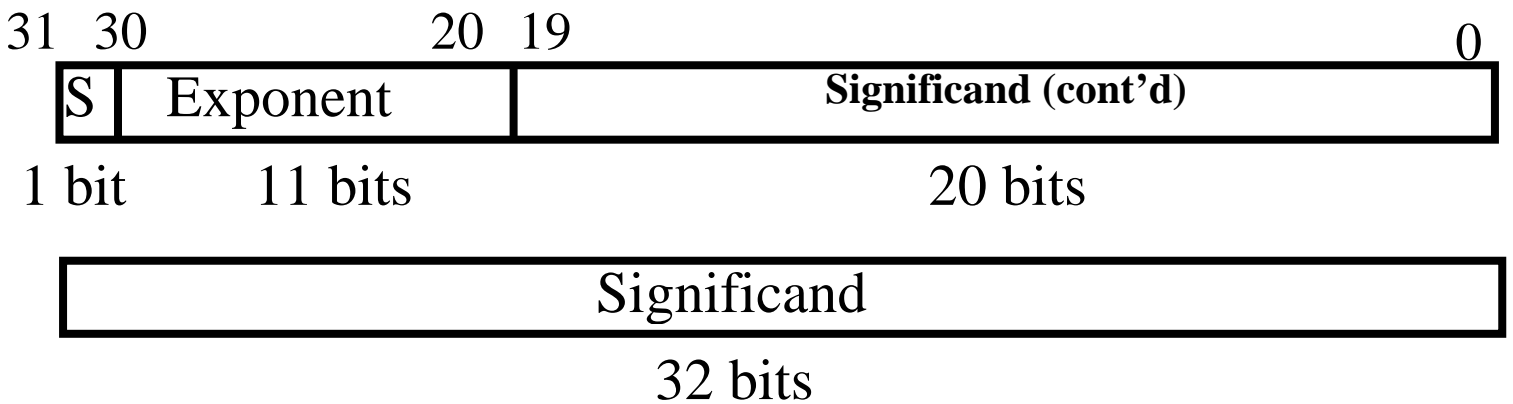

Double Precision (vs. Single Precision)

C variable declared as doubleRepresent numbers almost as small as 2.0×10^{-308}

to almost as large as 2.0×10^{308}

But primary advantage is greater accuracy due to larger significand

IEEE 754 Floating Point Standard

Single Precision, Double Precision similar
Sign bit: 1 means -ve and 0 means +ve
Significand: To pack more bits, leading 1 implicit for normalized numbers
1 + 23 bits single, 1 + 52 bits double
Always true: Significand < 1
(for normalized numbers)

Called Biased Notation, where bias is number to be subtracted to get the real number

IEEE 754 uses bias of 127 for single precision.

Subtract 127 from Exponent field to get actual value for exponent.

$$(-1)^S \times (1 + \text{Significand}) \times 2^{(\text{Exponent}-127)}$$

1023 is bias for double precision

Understanding FP Numbers

Ist Method (Fractions):

In decimal: $0.340_{10} \Rightarrow 340_{10}/1000_{10}$
 $\Rightarrow 34_{10}/100_{10}$

In binary: $0.110_2 \Rightarrow 110_2/1000_2 = 6_{10}/8_{10}$
 $\Rightarrow 11_2/100_2 = 3_{10}/4_{10}$

Advantage: Less purely numerical, more thought oriented; this method usually helps people understand the meaning of the significand better.

2nd Method (Place Values):

Convert from scientific notation

In decimal: $1.6732 = (1 \times 10^0) + (6 \times 10^{-1}) +$
 $(7 \times 10^{-2}) + (3 \times 10^{-3}) + (2 \times 10^{-4})$

In binary: $1.1001 = (1 \times 2^0) + (1 \times 2^{-1}) +$
 $(0 \times 2^{-2}) + (0 \times 2^{-3}) + (1 \times 2^{-4})$

Interpretation of value in each position extends beyond the decimal/binary point

Advantage: Good for quickly calculating the significand value; use this method for translating FP numbers

Example

Converting Binary FP to Decimal

0	0110 1000	101 0101 0100 0011 0100 0010
---	-----------	------------------------------

Sign: 0 => positive

Exponent:

$$0110\ 1000_{\text{two}} = 104_{\text{ten}}$$

$$\text{Bias adjustment: } 104 - 127 = -23$$

Significand:

$$1 + 1 \times 2^{-1} + 0 \times 2^{-2} + 1 \times 2^{-3} + 0 \times 2^{-4} + 1 \times 2^{-5} + \dots$$

$$= 1 + 2^{-1} + 2^{-3} + 2^{-5} + 2^{-7} + 2^{-9} + 2^{-14} + 2^{-15} + 2^{-17} + 2^{-22}$$

$$= 1.0_{\text{ten}} + 0.666115_{\text{ten}}$$

$$\text{Represents: } 1.666115_{\text{ten}} \times 2^{-23} \sim 1.986 \times 10^{-7}$$

(about 2/10,000,000)

Converting Decimal to FP

Simple Case: If denominator is exponent of 2 (2, 4, 8, 16, etc.), then it's easy.

Show MIPS representation of -0.75

$$= -3/4$$

$$-11_{\text{two}}/100_{\text{two}} = -0.11_{\text{two}}$$

Normalized to $-1.1_{\text{two}} \times 2^{-1} (-1)^S \times$
 $(1 + \text{Significand}) \times 2^{(\text{Exponent}-127)}$

$$(-1)^1 \times (1 + .100\ 0000 \dots 0000) \times 2^{(126-127)}$$

1	0111 1110	100 0000 0000 0000 0000 0000
---	-----------	------------------------------

Converting Decimal to FP

Not So Simple Case:

If denominator is not an exponent of 2.

Then we can not represent number precisely, but that's why we have so many bits in significand: for precision

Once we have significand, normalizing a number to get the exponent is easy.

So how do we get the significand of a never-ending number?

- *All rational numbers have a repeating pattern when written out in decimal.*
- *This also applies in binary.*

To finish conversion:

- Write out binary number with repeating pattern.
- Cut it off after correct number of bits (Different for single vs. double precision)
- Derive Sign, Exponent and Significand fields.

Example

What is the decimal equivalent of the floating point number given below:

1	1000 0001	111 0000 0000 0000 0000 0000
---	-----------	------------------------------

S Exponent

Significand

$$(-1)^S \times (1 + \text{Significand}) \times 2^{(\text{Exponent}-127)}$$

$$(-1)^1 \times (1 + .111) \times 2^{(129-127)}$$

$$-1 \times (1.111) \times 2^{(2)}$$

$$-111.1$$

$$-7.5$$